


14:332:231 DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University
Electrical & Computer Engineering
Fall 2013

Lecture #10: Decoders

General Decoder Structure

 
- A decoder is a logic circuit that converts coded inputs into coded outputs.
- Each input code word produces a different output code word (there is a one-to-one mapping between inputs and outputs)



2 of 20

Decoder Example

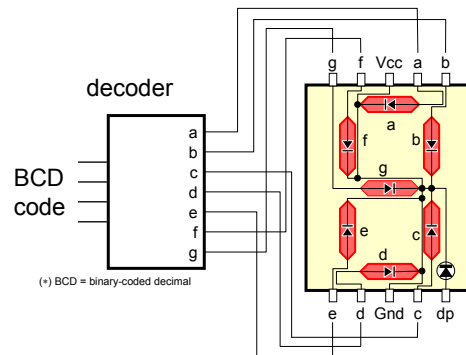
- BCD to seven-segment decoder
 - has 4-bit BCD as input code and the “seven-segment code” as its output code



3 of 20

Binary Decoder


 
- Accepts a n -bit binary input code and generates a 1-out-of- 2^n output code
- Used to activate exactly one of 2^n outputs based on n -bit input value
- Examples: 2-to-4, 3-to-8, 4-to-16, etc.
- Note: BCD to seven-segment decoder is NOT a binary decoder
 - Because multiple outputs active simultaneously
- Binary decoders are simple and general; can be used to build general decoders (shown later)



4 of 20


Gate Level Implementation of Decoders

1:2 decoders

  


2:4 decoders

active-high enable:

 

active-low enable:

 



5 of 20

How It Works

2:4 decoder:


- input combination: "00"
- output: O_0

- input combination: "10"
- output: O_2

  

6 of 20

Binary 2-to-4 Decoder

 

Inputs			Outputs			
EN	I1	I0	Y3	Y2	Y1	Y0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0


Note "x" (don't care) notation.

- Note that the outputs of the decoder correspond to the *minterms*: $Y_i = m_i$
 - e.g., $Y_0 = I_1' \cdot I_0'$
 - $Y_1 = I_1' \cdot I_0$ etc.

7 of 20

MSI 2-to-4 Decoder

 
(* COMPARE TO Wakerly, 4th edition, Figure 6-32(b), page 385)



- Input buffering (less load on input circuit)
- NAND gates (faster operation)

8 of 20

Complete 74x139 Decoder

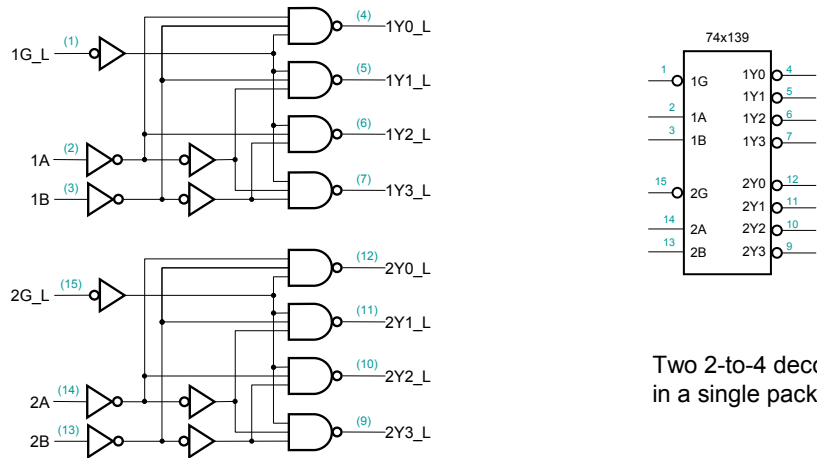

Two 2-to-4 decoders
in a single packaging

(* COMPARE TO 74x138 3-to-8 decoder, described next)


9 of 20

74x138: 3-to-8 decoder

- Commercially available MSI 3-to-8 decoder
 - Note that its outputs are active low
 - » because TTL and CMOS *inverting* gates are faster than non-inverting gates

- Logic equations for internal output signals include “enable” signals.
- Example:
 
$$Y_5 = \underbrace{G_1 \cdot G_2A \cdot G_2B}_{\text{enable}} \cdot \underbrace{C \cdot B' \cdot A}_{\text{select}}$$



10 of 20

Truth Table for a 3-to-8 Decoder

Inputs						Outputs							
G1	G2A_L	G2B_L	C	B	A	Y7_L	Y6_L	Y5_L	Y4_L	Y3_L	Y2_L	Y1_L	Y0_L
0	x	x	x	x	x	1	1	1	1	1	1	1	1
x	1	x	x	x	x	1	1	1	1	1	1	1	1
x	x	1	x	x	x	1	1	1	1	1	1	1	1
1	0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	0	1	1	1	1	1	1	1	0	1
1	0	0	0	1	0	1	1	1	1	1	0	1	1
1	0	0	0	1	1	1	1	1	1	0	1	1	1
1	0	0	1	0	0	1	1	1	0	1	1	1	1
1	0	0	1	0	1	1	1	0	1	1	1	1	1
1	0	0	1	1	0	1	0	1	1	1	1	1	1
1	0	0	1	1	1	0	1	1	1	1	1	1	1

- Because of the inversion bubbles, we have the following relations between internal and external signals


$$G2A = G2A_L'$$

$$Y5 = Y5_L'$$

etc.

11 of 20

3-to-8 Decoder Logic Diagram

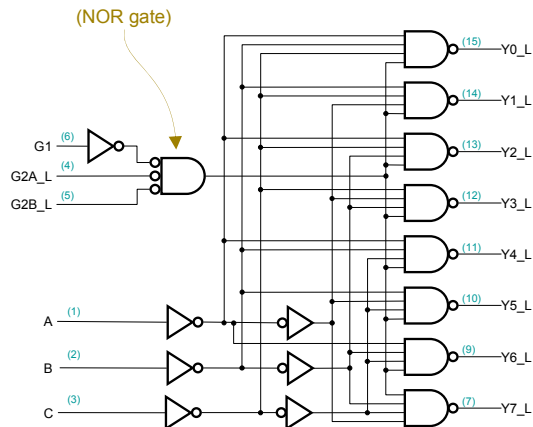


12 of 20

Decoder Cascading

- Decoders can be cascaded hierarchically to decode larger code words

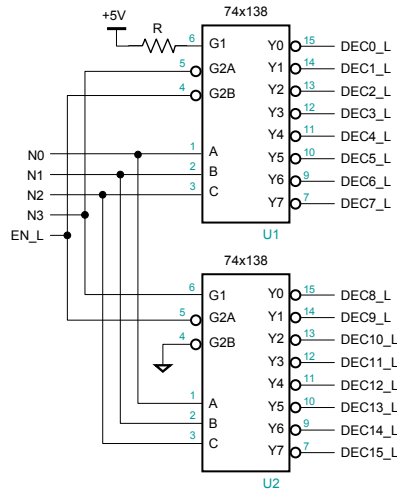
- Example:
Design a 4-to-16 decoder using
74x128s (3-to-8 decoders)



13 of 20

More Cascading

5-to-32 decoder

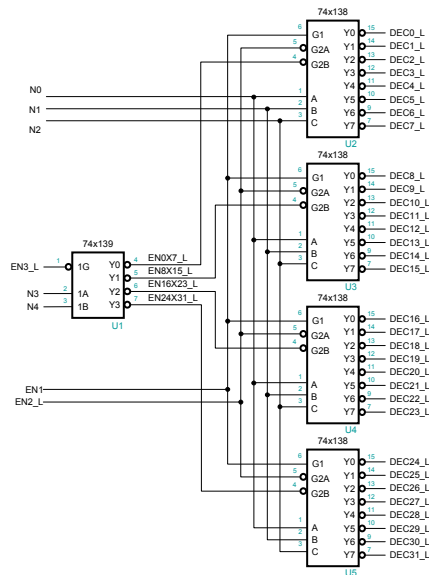

14 of 20


Decoder Applications

- Microprocessor memory systems
 - Selecting different banks of memory
- Microprocessor input/output systems
 - Selecting different devices
- Microprocessor instruction decoding
 - Enabling different functional units
- Memory chips
 - Enabling different rows of memory depending on address
- Lots of other applications

15 of 20

Decoders as General-Purpose Logic

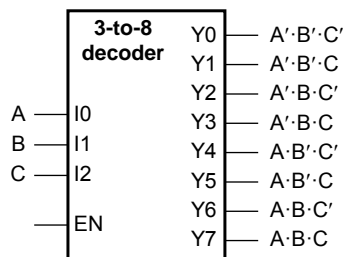- n -to- 2^n decoders can implement any function of n variables
 - with the variables used as control inputs
 - the appropriate *minterms* summed to form the function



decoder generates appropriate *minterm* based on *control signals* (it “decodes” control signals)


16 of 20

Decoders as General-Purpose Logic

■ $F1 = A' \cdot B \cdot C' \cdot D + A' \cdot B' \cdot C \cdot D + A \cdot B \cdot C \cdot D$

■ $F2 = A \cdot B \cdot C' \cdot D' + A \cdot B \cdot C$

■ $F3 = A' + B' + C' + D'$

 


17 of 20

Customized Decoder Circuit

CS_L	RD_L	A2	A1	A0	Output(s) to Assert
1	x	x	x	x	none
x	1	x	x	x	none
0	0	0	0	0	BILL_L, MARY_L
0	0	0	0	1	MARY_L, KATE_L
0	0	0	1	0	JOAN_L
0	0	0	1	1	PAUL_L
0	0	1	0	0	ANNA_L
0	0	1	0	1	FRED_L
0	0	1	1	0	DAVE_L
0	0	1	1	1	KATE_L

Truth table

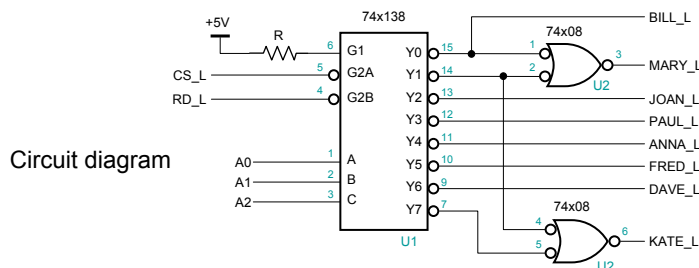


Circuit diagram



18 of 20

Decoder-Based Circuits

 Designing a circuit for the logic function
 $F = \sum_{X,Y,Z} (0,2,3,5)$:



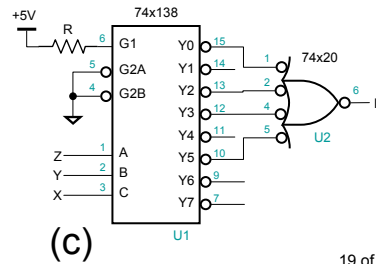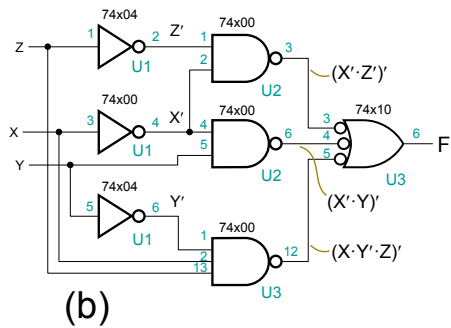- (a) Karnaugh map;
- (b) NAND-based minimal sum-of-products;
- (c) decoder-based canonical sum.



Multiple Decoding w/ a Single Decoder

