


14:332:231 DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University
Electrical & Computer Engineering
Fall 2013

Lecture #12: Multiplexers, Exclusive OR Gates, and Parity Circuits

Multiplexers (Data Selectors)

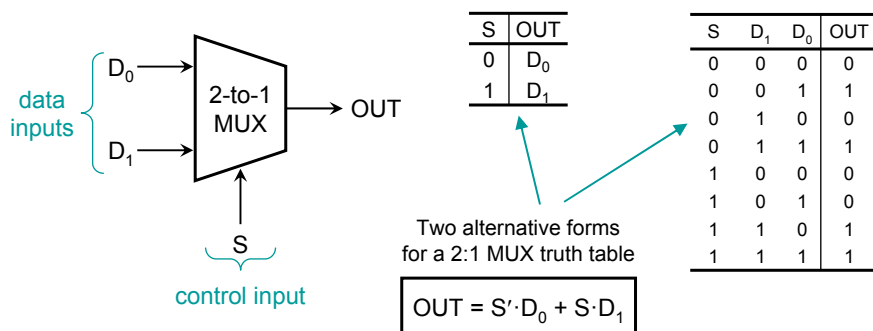
- A multiplexer (MUX for short) is a *digital switch*:
 - it passes (connects) one of its data inputs to the output
 - the data input selected is a function of a set of control inputs called *selection inputs*



2 of 31


Multiplexers Do Selecting

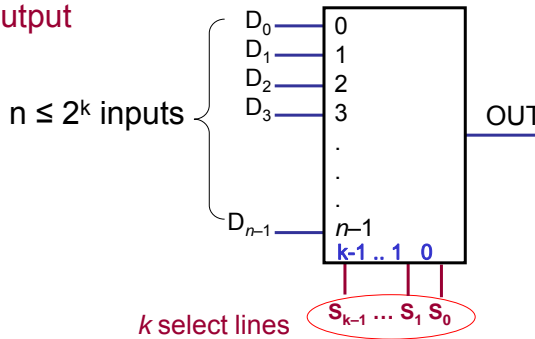- Selecting of data or information is a critical function in digital systems and computers
- Circuits that perform selecting have:
 - A set of n information **inputs** D_i from which the selection is made
 - A set of k **control (select) lines** for making the selection
 - A **single output**



3 of 31

Multiplexer Analogy

 

(Source: F. Vahid, "Digital Design", J. Wiley, 2007)

4 of 31


Example Uses of Multiplexers

- In computers to select among signals


- To implement command:

if $A=0$ then $Z=X \cdot Y$

else $Z=X \oplus Y$

 

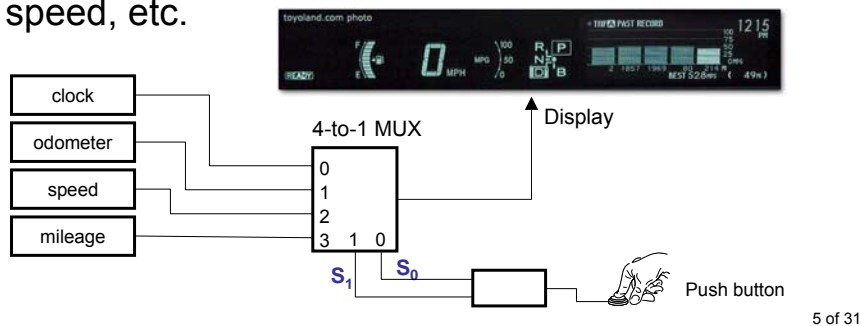- Trip controller in a car to display mileage, time, speed, etc.





5 of 31

Multiplexer Structure

- Switch circuit equivalent

- Multiplexer is unidirectional

 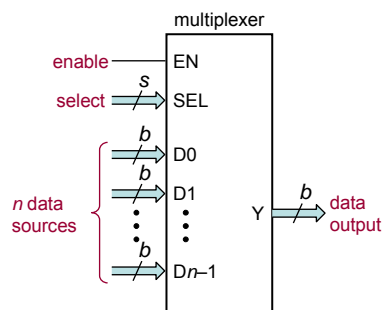

6 of 31

Example: 4-to-1-line Multiplexer

- Expression for OUT:

$$\text{OUT} = \underbrace{S_1' \cdot S_0'}_{M_0} \cdot D_0 + \underbrace{S_1' \cdot S_0}_{M_1} \cdot D_1 + \underbrace{S_1 \cdot S_0'}_{M_2} \cdot D_2 + \underbrace{S_1 \cdot S_0}_{M_3} \cdot D_3$$

$$\text{or: } \text{OUT} = \sum_{j=0}^{2^k-1} M_j \cdot D_j$$


S_1	S_0	OUT
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

- Circuit implementation: Sum-of-Products
 - 4 AND gates (4 product terms)
 - 2-to-4 line decoder (to generate the **minterms**)

7 of 31

Example: 4-to-1-line Multiplexer

- 2-to-2²-line decoder
- 2² × 2 AND-OR

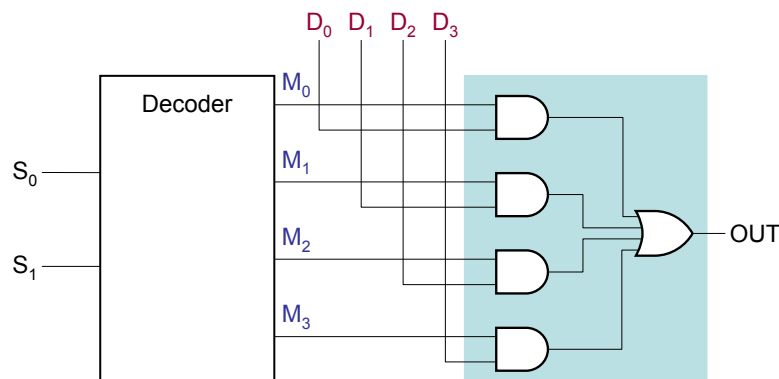

8 of 31

General Multiplexer Equation

- A general logic equation for a multiplexer output:



$$iY = \sum_{j=0}^{n-1} EN \cdot M_j \cdot iD_j$$

- Logical sum of product terms
- Variable iY is a particular output bit ($1 \leq i \leq b$)
- M_j is a minterm j of the s select inputs



9 of 31

Gate Level Implementation of MUXs

- 2:1 MUX

  

- 4:1 MUX

  

10 of 31

Multiplexer Standard Packaging

IC has limited number of pins (16)

$$n \cdot b + b + s + 1 \leq 16 - 2$$

n in *b* out *s* SEL EN

n data inputs
b bits per input
s select inputs

$$(n+1) \cdot b + \lceil \log_2 n \rceil \leq 13$$

b n s

1	8	3	(12)	8 input 1 bit	74x151
2	4	2	(12)	dual 4 input 2 bit	74x153
4	2	1	(13)	quad 2 input 4 bit	74x157

11 of 31

Truth table of 74x151



- Truth table for 74x151 8-input, 1-bit multiplexer
- Only “control” inputs are listed under “Inputs”
- Outputs specified as “0” or “1”, or a simple logic function of “data” inputs (e.g., D0 or D0’)

Inputs				Outputs		
EN	L	S2	S1	S0	Y	Y_L
1	x	x	x	x	0	1
0	0	0	0	0	D0	D0'
0	0	0	0	1	D1	D1'
0	0	0	1	0	D2	D2'
0	0	0	1	1	D3	D3'
0	1	0	0	0	D4	D4'
0	1	0	0	1	D5	D5'
0	1	0	1	0	D6	D6'
0	1	0	1	1	D7	D7'

12 of 31

74x151 8-input 1-bit Multiplexer



- 74x151 logic diagram and logic symbol

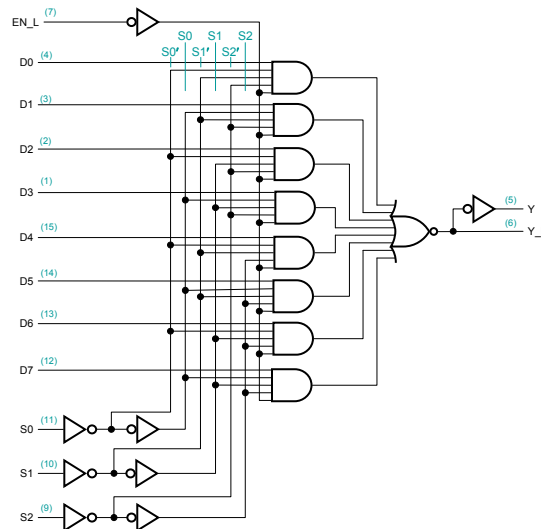 

13 of 31

74x157 2-input 4-bit Multiplexer

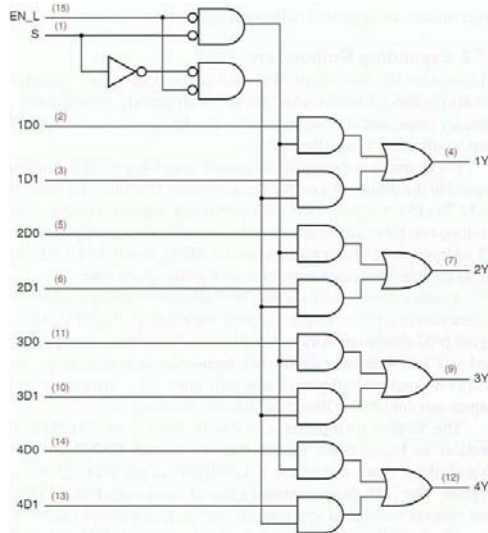 - 74x157 selects between two 4-bit inputs




14 of 31

74x157 2-input 4-bit Multiplexer

- 74x157 truth table:


Inputs		Outputs			
EN_L	S	1Y	2Y	3Y	4Y
1	x	0	0	0	0
0	0	1D0	2D0	3D0	4D0
0	1	1D1	2D1	3D1	4D1

 

15 of 31


Cascading/Expanding Multiplexers

 - Large multiplexers can be made by cascading smaller ones



Control signals **S1** and **S0** simultaneously choose one of **D0, D1, D2, D3** and one of **D4, D5, D6, D7**

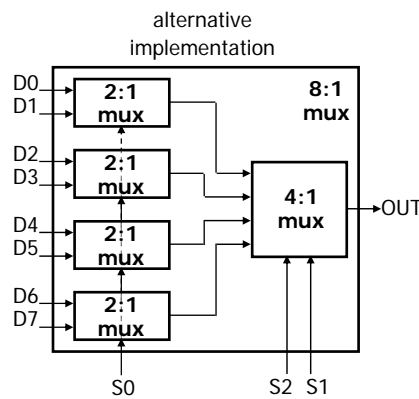
Control signal **S2** chooses which of the upper or lower mux's output to gate to OUT



16 of 31

Cascading/Expansion

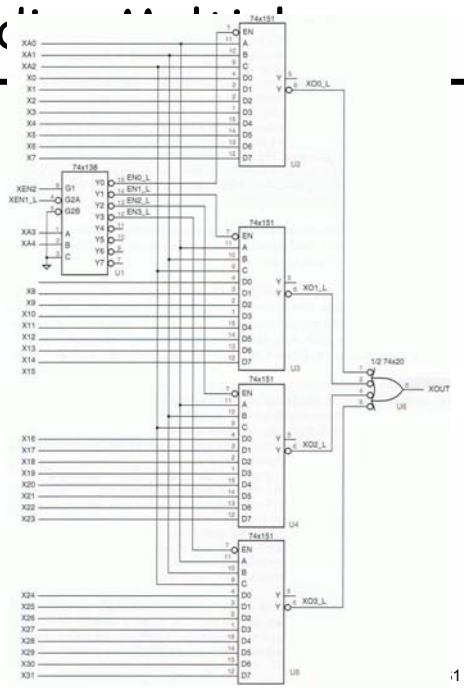- Combining four 74x151s to make a 32-to-1 multiplexer
- 74x138 3-to-8 decoder used as 2-to-4 decoder for two high-order bits to enable one of 74x151s



Multiplexers as General-purpose Logic


- A $2^n:1$ multiplexer can implement any function of n variables

- with the variables used as control inputs and
- the data inputs tied to 0 or 1

 - Example:


$$\begin{aligned}
 F(A,B,C) &= M_0 + M_2 + M_6 + M_7 \\
 &= A' \cdot B' \cdot C' + A' \cdot B \cdot C' + A \cdot B' \cdot C' + A \cdot B \cdot C \\
 &= A' \cdot B' \cdot C' \cdot (1) + A' \cdot B' \cdot C \cdot (0) + A' \cdot B \cdot C' \cdot (1) + A' \cdot B \cdot C \cdot (0) + \\
 &\quad A \cdot B' \cdot C' \cdot (0) + A \cdot B' \cdot C \cdot (0) + A \cdot B \cdot C' \cdot (1) + A \cdot B \cdot C \cdot (1)
 \end{aligned}$$

$$\text{OUT} = A' \cdot B' \cdot C' \cdot I_0 + A' \cdot B' \cdot C \cdot I_1 + A' \cdot B \cdot C' \cdot I_2 + A' \cdot B \cdot C \cdot I_3 + \\
 A \cdot B' \cdot C' \cdot I_4 + A \cdot B' \cdot C \cdot I_5 + A \cdot B \cdot C' \cdot I_6 + A \cdot B \cdot C \cdot I_7$$



Multiplexers as General-purpose Logic

 - Generalization:**
 data inputs can also be tied to variables not just 0's and 1's




19 of 31

Multiplexers as Function Generators

- We can generate the four possible Z values (0, 1, Z, Z') and realize the function with half the values
- Realizing $F = \sum_{X,Y,Z} (0,3,5,6)$ with a 4-input multiplexer:

Row	X	Y	Z	F
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

 


20 of 31

4-variable Function using 8-input Multiplexer

- Realizing $F = \sum_{N_0, N_1, N_2, N_3} (1, 2, 3, 5, 7, 11, 13)$ with an 8-input multiplexer:


Row	N_3	N_2	N_1	N_0	F
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	0

 

21 of 31

Demultiplexers

 
- Route a single input to one of many outputs, as a function of a set of control inputs



22 of 31

Demultiplexers

 
- Demultiplexer function is just the inverse of multiplexer's
- A *binary decoder* with enable input can be used as a demultiplexer



23 of 31

Demultiplexer Analogy


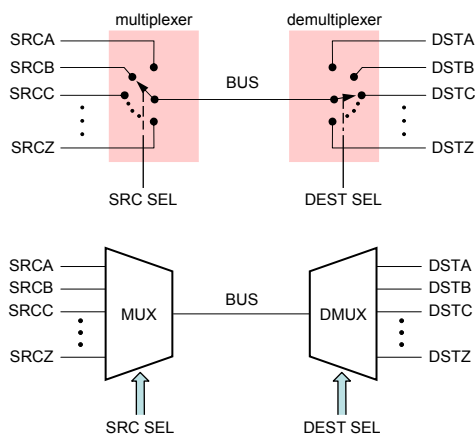
- A MUX driving a bus and a demultiplexer receiving the bus



24 of 31

Exclusive-OR Gates

- **Exclusive-OR (XOR)** gate is a 2-input gate whose output is “1” if exactly one of its input is “1”
 - or: XOR gate produces a “1” output if its inputs are *different*
- **Exclusive-NOR (XNOR) or Equivalence** just opposite—produces output “1” if its inputs are the same

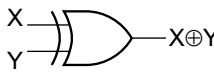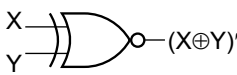- XOR: $X \oplus Y = X' \cdot Y + X \cdot Y'$ 
- XNOR: $(X \oplus Y)' = X \cdot Y + X' \cdot Y'$ 


25 of 31

Exclusive-OR Gates


- Truth table and gate-level implementation

X	Y	$X \oplus Y$ (XOR)	$(X \oplus Y)'$ (XNOR)
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

AND-OR implementation:

 

three-level NAND implementation:

 

$$(X \cdot Y)' \cdot (X + Y) = (X' + Y') \cdot (X + Y) = X' \cdot Y + Y' \cdot X$$

26 of 31

XOR versus XNOR

$$\begin{aligned}(X \oplus Y)' &= (X' \cdot Y + X \cdot Y')' = (X + Y') \cdot (X' + Y) \\ &= X \cdot X' + X' \cdot Y' + X \cdot Y + Y' \cdot Y \\ &= X \cdot Y + X' \cdot Y'\end{aligned}$$

$X \rightarrow X'$ $\text{out} \rightarrow \text{out}'$... the circuit XOR = XNOR
 $(X' \cdot Y' + X \cdot Y)' = X' \cdot Y + X \cdot Y'$


$X \rightarrow X'$ $\text{out} \rightarrow \text{out}'$... the circuit XNOR = XOR
 $X' \cdot Y' + X \cdot Y$

$$X \oplus 1 = X \cdot 0 + X' \cdot 1 = X'$$


27 of 31

Equivalent Symbols for XOR/XNOR

- XOR gates

 

- XNOR gates

 

- Simple rule:


- Any two signals (inputs or output) of an XOR or XNOR gate may be complemented w/o changing the resulting logic function

$$X \oplus 0 = X \quad X \oplus 1 = X'$$


28 of 31

Cascading XOR gates

■ Daisy-chain connection

 

■ Balanced tree structure

 

29 of 31


Cascading XOR gates

- The tree structure is faster than daisy-chain connection because the gates depth of its treelike structure is $\log_2(N)$, which is much less than $N-1$ for a daisy-chain structure
- Both are called **odd-parity circuits** because its output is “1” if an *odd number of inputs* are “1”
 - Used to generate and check parity bits in computer systems
 - Detects any single-bit error
- **Even-parity circuit** has odd-parity circuit’s output inverted—its output is “1” if an *even number* of its inputs are “1”

30 of 31

 Example Parity Computation

$$F = I1 \oplus I2 \oplus I3 \quad F = 1 \quad \text{ODD number of "1" in the input}$$



I1	I2	I3	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

31 of 31