

14:332:231  
DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University  
Electrical & Computer Engineering  
Fall 2013


Lecture #13: Digital Comparators

## Digital Comparators

- **Comparator**: A circuit that compares two binary words and indicates whether they are equal
- **Magnitude comparator**: Interprets its inputs as signed or unsigned numbers and indicates their arithmetic relationship (greater or less than)
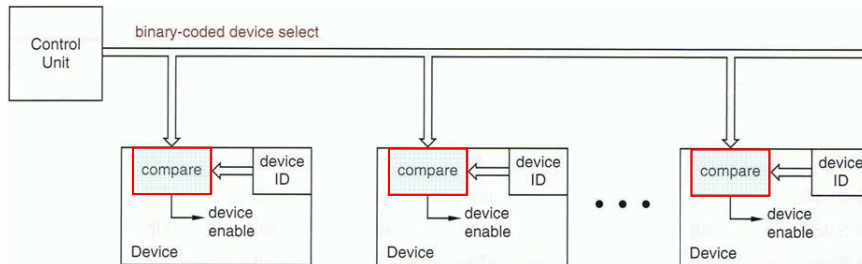
# Example Comparator Use

- Devices are enabled by comparing a “device select” word with a predetermined “device ID”




3 of 12

# Equality Comparators

 
## 1-bit comparator

- Active-high output (DIFF) asserted if the inputs are different


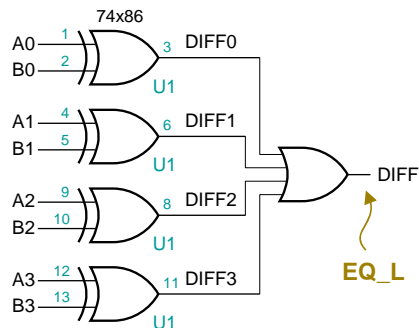
## 4-bit comparator

- The DIFF output is asserted if *any* of the input pairs are different



4 of 12

# 4-Bit Magnitude Comparator

- Two input numbers to compare, 4 bits each:  $A=A_3A_2A_1A_0$ ;  $B=B_3B_2B_1B_0$
- Three outputs, reporting "greater than", "less than", and "equal", respectively

Compared Inputs				Outputs		
A3, B3	A2, B2	A1, B1	A0, B0	"A > B"	"A < B"	"A = B"
$A_3 > B_3$	x	x	x	1	0	1
$A_3 < B_3$	x	x	x	0	1	0
$A_3 = B_3$	$A_2 > B_2$	x	x	1	0	0
$A_3 = B_3$	$A_2 < B_2$	x	x	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 > B_1$	x	1	0	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 < B_1$	x	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 > B_0$	1	0	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 < B_0$	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	1	0	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	0	0	1



Note "x" (don't care) notation.

5 of 12
 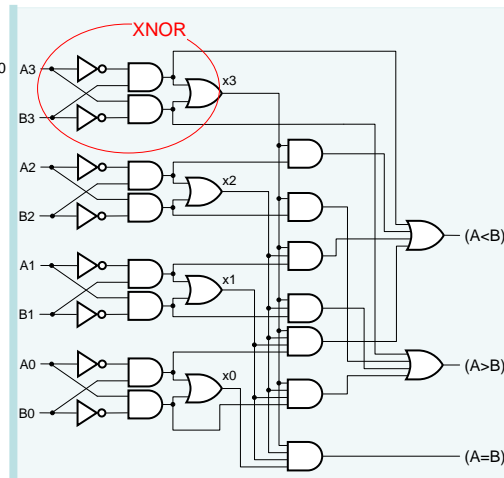
# 4-Bit Magnitude Comparator

- Input  $A=A_3A_2A_1A_0$ ;  $B=B_3B_2B_1B_0$
- Case  $A = B$ :  $A_3=B_3, A_2=B_2, A_1=B_1, A_0=B_0$   
 $x_i = (A_i \oplus B_i)' = A_i \cdot B_i + A_i' \cdot B_i'$   


$$\begin{aligned} \text{XNOR} &= (A_i \oplus B_i)' = (A_i \cdot B_i + A_i' \cdot B_i')' \\ &= (A_i \cdot B_i)' \cdot (A_i' \cdot B_i')' \\ &= A_i' \cdot A_i + A_i' \cdot B_i' + A_i \cdot B_i + B_i \cdot B_i' \\ &= A_i \cdot B_i + A_i' \cdot B_i' \end{aligned}$$
  - Output:  $x_3 \cdot x_2 \cdot x_1 \cdot x_0$
- Case  $A > B$ :  
  - Output:  $A_3 \cdot B_3' + x_3 \cdot A_2 \cdot B_2' + x_3 \cdot x_2 \cdot A_1 \cdot B_1' + x_3 \cdot x_2 \cdot x_1 \cdot A_0 \cdot B_0'$
- Case  $A < B$ :  
  - Output:  $A_3' \cdot B_3 + x_3 \cdot A_2' \cdot B_2 + x_3 \cdot x_2 \cdot A_1' \cdot B_1 + x_3 \cdot x_2 \cdot x_1 \cdot A_0' \cdot B_0$



6 of 12
 
# Iterative Combinational Circuits


- General structure:  $n$  identical modules
  - For problems that can be solved by an iterative algorithm:
    1. Set  $C_0$  to its initial value and set  $i$  to 0
    2. While  $i < n$  repeat:
      - a) Use  $C_i$  and  $PI_i$  to determine the values of  $PO_i$  and  $C_{i+1}$
      - b) Increment  $i$




7 of 12

# An Iterative Comparator Circuit

 - (a) module for one bit
- (b) complete circuit
  - Comparing two  $n$ -bit values  $X$  and  $Y$ :
    1. Set  $EQ_0$  to 1 and set  $i$  to 0
    2. While  $i < n$  repeat:
      - a) If  $EQ_i$  is 1 and  $X_i$  equals  $Y_i$ , set  $EQ_{i+1}$  to 1  
Else set  $EQ_{i+1}$  to 0
      - b) Increment  $i$
- Slow because the cascading signals need time to “ripple” from left to right




$$EQ_0 = (A \oplus B) \cdot EQ_I$$

 

8 of 12
 
# 4-bit Comparator 74x85

- Outputs:
  - Greater-than output (AGTBOUT)
  - Less-than output (ALTBOUT)
  - Equal output (AEQBOUT)
- Cascading inputs:
  - AGTBIN, ALTBIN, AEQBIN
- Cascading inputs and the outputs are arranged in a 1-out-of-3 code, since normally exactly one input and output should be asserted




# 12-bit Comparator using 74x85s

$$\text{AGTBOUT} = (A > B) + (A = B) \cdot \text{AGTBIN}$$

$$\text{AGTBOUT} = (A = B) \cdot \text{AEQBIN}$$



$$\text{AGTBOUT} = (A < B) + (A = B) \cdot \text{ALTBIN}$$
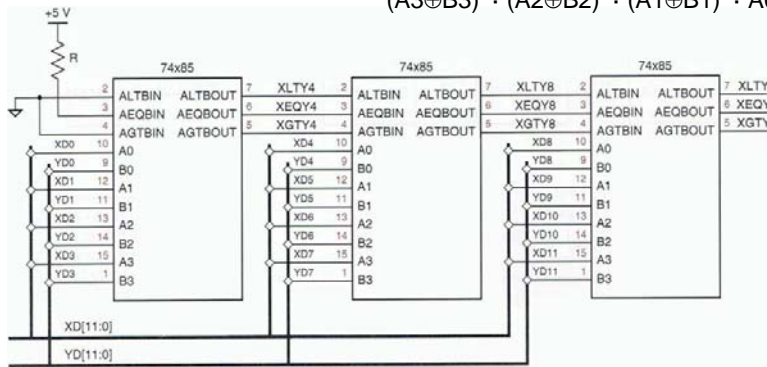
$$\begin{aligned} (A > B) = & A_3 \cdot B_3' + (A_3 \oplus B_3)' \cdot A_2 \cdot B_2' + \\ & (A_3 \oplus B_3)' \cdot (A_2 \oplus B_2)' \cdot A_1 \cdot B_1' + \\ & (A_3 \oplus B_3)' \cdot (A_2 \oplus B_2)' \cdot (A_1 \oplus B_1)' \cdot A_0 \cdot B_0' \end{aligned}$$


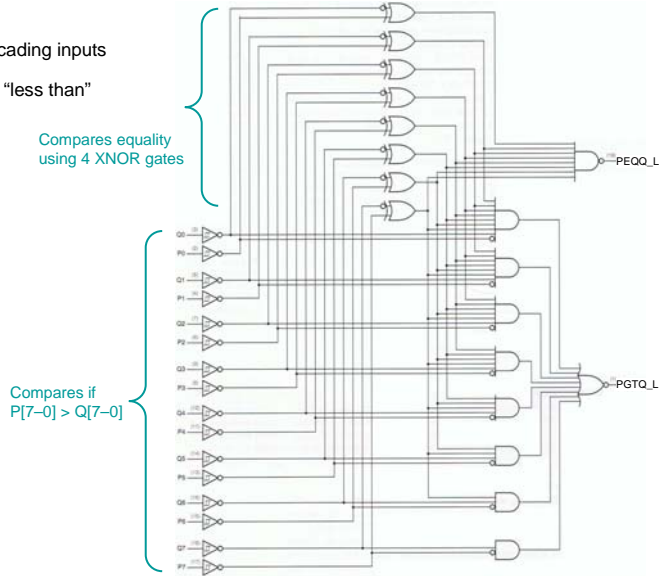 
# 8-bit Magnitude Comparator


- 74x682
  - Does not have cascading inputs (unlike 74x85)
  - Does not provide a "less than" output



11 of 12
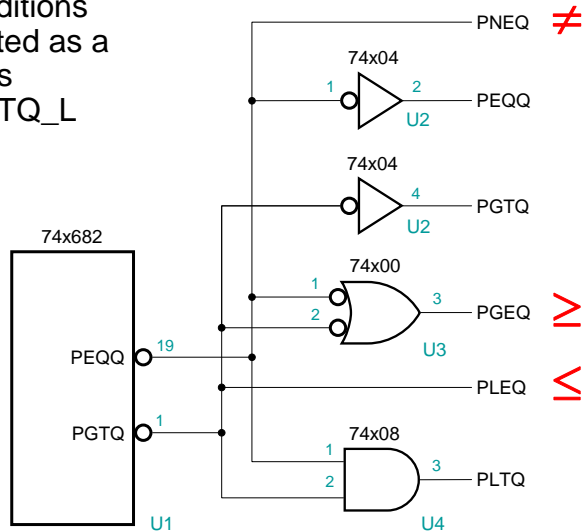
# Arithmetic Conditions from 74x682

- Not-provided conditions can be implemented as a function of outputs PEQQ\_L and PGTQ\_L



12 of 12