

14:332:231 DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University
Electrical & Computer Engineering
Fall 2013

Lecture #14: Adders, Subtractors, and ALUs

Binary Adder [Wakerly 4th Ed., Sec. 6.10, p. 474]

- Binary addition is used frequently
- Addition Development:
 - Single bit { – *Full-Adder* (FA), a 3-input bit-wise addition functional block,
 - Vector { – *Ripple Carry Adder*, an iterative array to perform binary addition, and
 - Improved adder { – *Carry-Look-Ahead Adder* (CLA), a hierarchical structure to improve performance (check in Wikipedia: http://en.wikipedia.org/wiki/Carry_look-ahead_adder).

Functional Block: Half Adder

- A 2-input, 1-bit width binary adder that performs the following computations:

X	0	0	1	1
+ Y	+ 0	+ 1	+ 0	+ 1
CO HS	0 0	0 1	0 1	1 0

- A half adder adds two bits to produce a two-bit sum
- The low-order bit is named “**half sum**” (HS), and the high-order bit is named “**carry out**” (CO)
- The half adder can be specified as a *truth table* for HS and CO →


X	Y	CO	HS
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

3 of 24

Half Adder

- Half-adder for 1-bit addends

X	Y	CO	HS
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


half sum:

$$HS = X \oplus Y$$

carry out:


$$CO = X \cdot Y$$

 

4 of 24

Full Adder [Recall Binary Addition from Lecture #2]

 - Basic building block is “full adder”
 - 1-bit-wide adder, produces sum and carry outputs
- Truth table:




Row	Inputs			Outputs	
	X	Y	Cin	S	Cout
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1


5 of 24

Full Adder from Half Adders

1-bit half adder

 

1-bit full adder

 

6 of 24

Full Adder

$$\begin{aligned}
 S &= HS \oplus CIN = X \oplus Y \oplus CIN = \overbrace{(X \cdot Y' + X' \cdot Y)}^{\text{first term}} \oplus CIN \\
 &= \underbrace{X \cdot Y' \cdot CIN' + X' \cdot Y \cdot CIN'}_{\text{first term direct}} + \underbrace{X' \cdot Y' \cdot CIN + X \cdot Y \cdot CIN}_{\text{first term complement}}
 \end{aligned}$$



$$\begin{aligned}
 COUT &= X \cdot Y + \underbrace{X \cdot CIN + Y \cdot CIN}_{\substack{\text{carry} \\ \text{generated} \\ \text{internally}}}
 \end{aligned}$$

7 of 24

Logic Optimization: Full Adder

Full adder Karnaugh map

Row	Inputs			Outputs	
	X	Y	Cin	S	Cout
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

  




$$S = X \cdot Y' \cdot CIN' + X' \cdot Y \cdot CIN' + X' \cdot Y' \cdot CIN + X \cdot Y \cdot CIN$$

$$Cout = X \cdot Y + X \cdot Cin + Y \cdot Cin$$

8 of 24

Full Adder Circuit

   - a) Gate-level circuit diagram
- b) Logic symbol
- c) Alternate logic symbol suitable for cascading



9 of 24


Subtraction

- Subtraction is the same as addition of the two's complement
- Recall Lecture #2:
The two's complement is the bit-by-bit complement plus 1
- Therefore, $X - Y = X + \bar{Y} + 1$
 - Complement Y inputs to adder, set first C_{in} to 1

10 of 24

Subtractor Design Using Adders


- Ripple subtractor

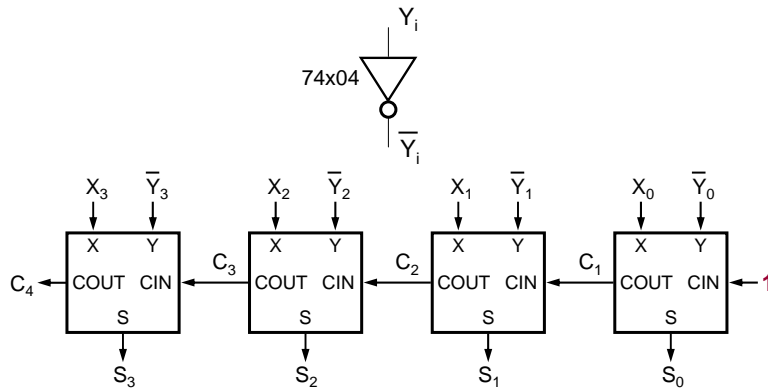

11 of 24

Subtractor Design Using Adders


- Ripple subtractor

 

12 of 24

2's Complement Adder/Subtractor

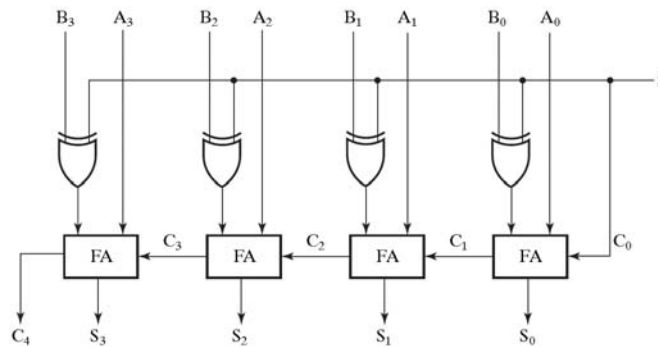- Subtraction can be done by addition of the 2's Complement.
 - Complement each bit (1's Complement.)
 - Add 1 to the result.
- The circuit shown computes both $A + B$ and $A - B$:
 - For $S = 1$, subtract, the 2's complement of B is formed by using XORs to form the 1's comp and adding the 1 applied to C_0 .
 - For $S = 0$, add, B is passed through unchanged



13 of 24

How to Detect Overflow

- Rule was: Sign of the two operands identical and *different* from the sign of the result [\[recall Lecture #3\]](#)
- Sign = most significant bit (MSB)

$$OVR = X_{n-1} \cdot Y_{n-1} \cdot S'_{n-1} + X'_{n-1} \cdot Y'_{n-1} \cdot S_{n-1}$$

or:

$$OVR = C_{n-1} \oplus C_n \quad \text{carry-in different from carry-out}$$

$$\begin{array}{r} 011\dots 1 \\ 000\dots 1 \\ \hline 100\dots 0 \end{array} \quad \begin{array}{r} 2^{n-1} - 1 \\ 1 \end{array}$$

$$OVR = 0 \cdot 0 \cdot 0 + 1 \cdot 1 \cdot 1 = 1 \quad \text{or}$$

$$OVR = 1 \oplus 0 = 1$$

14 of 24

Ripple Adder

- To add multiple operands, we “bundle” logical signals together into **vectors** and use *functional blocks* that operate on the vectors

- Example:
4-bit ripple carry adder:


Adds input vectors
A(3:0) and B(3:0) to get
a sum vector S(3:0)

- Note: carry-out of block i
becomes carry-in of block
 $i + 1$

Description	Bit index	Name
Carry in	0 1 1 0	C_i
Augend	1 0 1 1	A_i
Addend	0 0 1 1	B_i
Sum	1 1 1 0	S_i
Carry out	0 0 1 1	C_{i+1}

15 of 24

Ripple Adder

 

- It is relatively slow: For n bits, the worst case is:
- All of the adder's bits (and c_0) are present simultaneously

111... 1 -1
000... 1 +1

- $t_{ADD} = t_{XYC_{OUT}} + (n-2) \cdot t_{C_{IN}C_{OUT}} + t_{C_{IN}S}$

LSB (out C_1)

MSB (in C_{n-1})

- Carry look-ahead adders are the solution

16 of 24

Carry Lookahead Adder

- Uses a different circuit to calculate the carry out (calculates it *ahead* of the addition), to speed up the overall addition
- Requires more complex circuits
- Trade-off: **speed vs. area** (complexity, cost)

17 of 24

Carry Look-Ahead Addition

- **Carry generate:** input bits combination (x_i, y_i) that produces a carry-out of "1" ($c_{i+1} = 1$) independent of lower-order bits $(x_0 \dots x_{i-1}, y_0 \dots y_{i-1})$ and c_0 .
- **Carry propagate:** input bits combination (x_i, y_i) that produces a carry-out of "1" ($c_{i+1} = 1$) when $c_i = 1$.


Inputs			Outputs		
X	Y	Cin	S	Cout	
0	0	0	0	0	No carry
0	0	1	1	0	No carry
0	1	0	1	0	No carry
0	1	1	0	1	Carry propagated
1	0	0	1	0	No carry
1	0	1	0	1	Carry propagated
1	1	0	0	1	Carry generated
1	1	1	1	1	Carry generated & propagated

\uparrow C_i \uparrow C_{i+1}

$$g_i = x_i \cdot y_i \quad \leftarrow \text{carry-generate}$$

$$p_i = x_i + y_i \quad \leftarrow \text{carry-propagate}$$
 
$$\Rightarrow c_{i+1} = g_i + p_i \cdot c_i$$



Note that we could use half adder:
 $p_i^* = x_i \oplus y_i$

18 of 24

4-bit Carry Lookahead Adder


- Conceptual diagram

p_i^* see previous slide

$$s_i = HS_i \oplus c_i = p_i \oplus c_i$$

$$c_{i+1} = g_i + p_i \cdot c_i$$

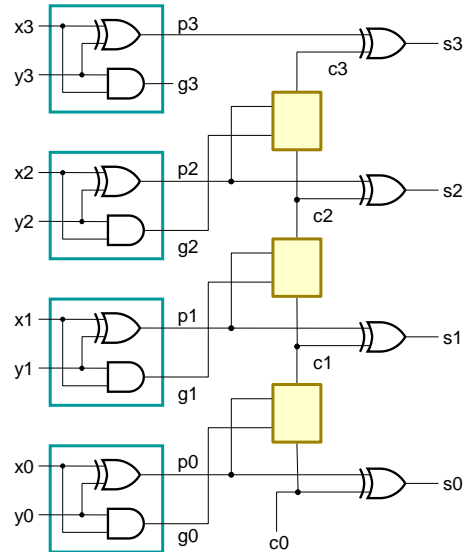Note that $g_i = 1 \Rightarrow p_i = 1$
(but not vice versa)
 $g_i \Rightarrow p_i \cdot g_i$




19 of 24

Carry Lookahead Logic

- Structure of one stage of a carry-lookahead adder:

$$g_i = x_i \cdot y_i \quad \leftarrow \text{carry-generate signal}$$
 
$$p_i = x_i + y_i \quad \leftarrow \text{carry-propagate signal}$$



20 of 24

Carry equations for first 4 adder stages

$$C_1 = p_0 \cdot (g_0 + c_0)$$

$$\begin{aligned} C_2 &= p_1 \cdot (g_1 + c_1) \\ &= p_1 \cdot (g_1 + p_0 \cdot (g_0 + c_0)) \\ &= p_1 \cdot (g_1 + p_0) \cdot (g_0 + c_0) \quad \text{distributivity theorem} \end{aligned}$$

$$\begin{aligned} C_3 &= p_2 \cdot (g_2 + c_2) \\ &= p_2 \cdot (g_2 + p_1 \cdot (g_1 + p_0) \cdot (g_0 + c_0)) \\ &= p_2 \cdot (g_2 + p_1) \cdot (g_1 + p_0) \cdot (g_0 + c_0) \end{aligned}$$

$$\begin{aligned} C_4 &= p_3 \cdot (g_3 + c_3) \\ &= p_3 \cdot (g_3 + p_2 \cdot (g_2 + p_1) \cdot (g_1 + p_0) \cdot (g_0 + c_0)) \\ &= p_3 \cdot (g_3 + p_2) \cdot (g_2 + p_1) \cdot (g_1 + p_0) \cdot (g_0 + c_0) \end{aligned}$$



21 of 24

74x283 4-bit Adder

- Uses carry lookahead (CLA) internally
- Differences from general CLA design:
 - Active-low versions of carry-generate (g_i') and carry-propagate (p_i') (b/c inverting gates are faster)
 - Algebraic manipulation of the half-sum:


$$\begin{aligned} hs_i &= x_i \oplus y_i = x_i \cdot y_i' + x_i' \cdot y_i \\ &= (x_i + y_i) \cdot (x_i' + y_i') \\ &= (x_i + y_i) \cdot (x_i \cdot y_i)' \\ &= p_i \cdot g_i' \end{aligned}$$
 - Creates the carry signals using INVERT-OR-AND (has \approx delay as a single inverting gate):
  
$$\begin{aligned} c_{i+1} &= p_i \cdot g_i + p_i \cdot c_i \\ &= p_i \cdot (g_i + c_i) \end{aligned}$$
- See Wakerly 4th ed., page 481, for carry equations



22 of 24


74x283 4-bit Adder (detail)

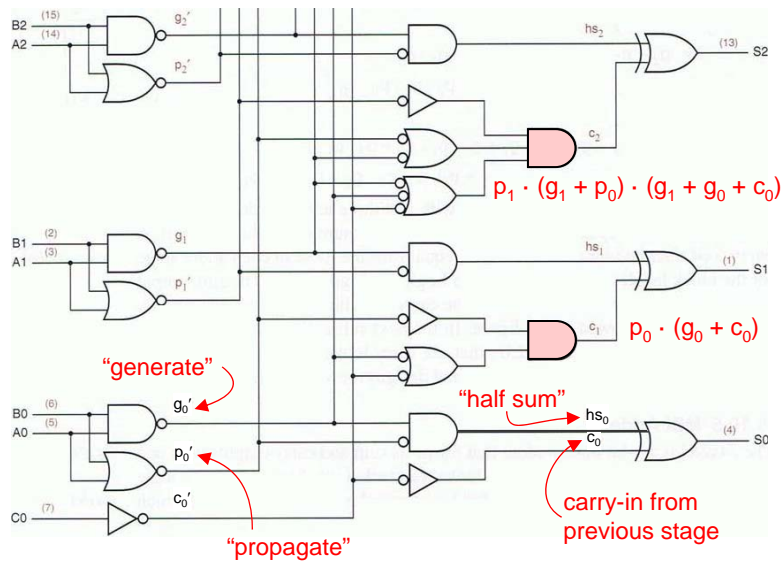

23 of 24

16-bit Group-ripple Adder

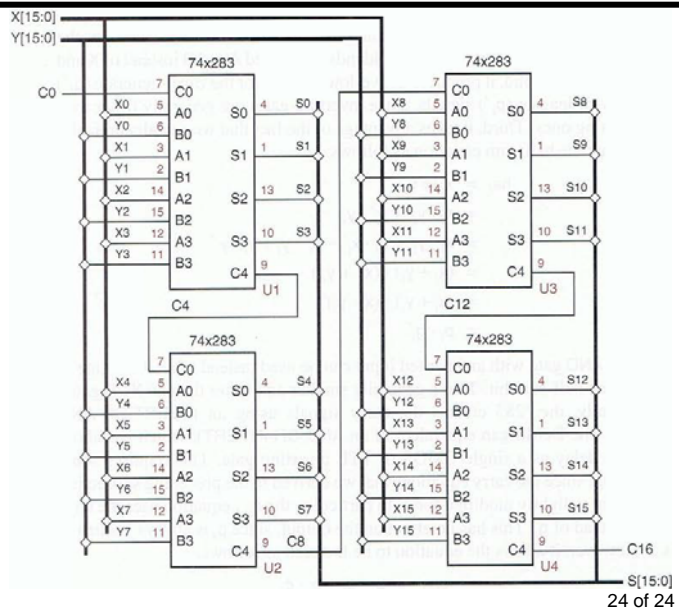- Ripple carry between groups
- Total propagation delay ≈ 8 inverting gates



24 of 24