

14:332:231 DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University
Electrical & Computer Engineering
Fall 2013


Lecture #15: Sequential Circuits: Latches

Sequential Circuits

- *Combinational circuits*: current input \rightarrow output
- *Sequential circuit*: current and past inputs \rightarrow output
- **Sequential circuits**
 - The information about the previous inputs history is called the “**state**” of the system
 - “State” is needed to predict the current and future behavior
 - *State variables* are bits of information *stored* in a memory (flip-flop) device n bits $\rightarrow 2^n$ states
 - A finite-state machine
 - Output depends on the current input *and* the past history represented by the states
 - Since n is always finite, sequential circuits are also called *finite state machines* (FSM)

2 of 29

Describing Sequential Circuits


 


- State table
 - For each current-state, specify next-states as function of inputs and current state
- State diagram
 - Graphical version of state table

3 of 29

Bistable Element

  
- The simplest sequential circuit
- Signal $B = A'$ appears after a short delay
 t_{pd} = propagation delay




4 of 29

Bistable Element

 - The simplest sequential circuit
- No input... for the moment
- Two states = one Boolean state variable, say, "Q"



"twisted"
representation:

 


(Q_L is active low)


5 of 29

Bistable Element

- Assume Q is equal "0"

 

 
- Bottom inverter's HIGH output → top inverter's input




→ Top inverter's output is forced LOW

Bistable Element

Assume Q is equal "0"

 



Now assume Q is equal "1"

 

7 of 29

Analog Analysis (1)

  - Assume pure CMOS thresholds, 5V is the V_{CC}
- Theoretical *threshold* center is 2.5V
- In principle, any TTL/CMOS have the same behavior, but different constants ...




[Recall Lecture #9]

8 of 29


Analog Analysis (2)

Assume threshold inputs at 2.5 V:

 

If nothing moves ...

 but a little input noise moves Q for example to ...




... Q is equal "1"

9 of 29

Metastability

 - Metastability is inherent in any bistable circuit



Transfer function:


$$\begin{aligned} V_{in1} &= V_{out2} \\ &= T(V_{in2}) \\ &= T(V_{out1}) \\ &= T(T(V_{in1})) \end{aligned}$$

$$V_{in2} = T(T(V_{in2}))$$

- Two stable points, one metastable point

10 of 29

Another Look at Metastability

 

- If the ball sits *exactly* on the top of the hill, the bistable circuit can be in metastable state until random noise *nondeterministically* chooses one of the stable states.
- Can appear in *any* sequential circuit, as we will see ...

11 of 29

Latches and Flip-Flops

- The two most popular varieties of elements used to build sequential circuits are: latches and flip-flops
 - Latch:** level sensitive storage element
 - Flip-Flop:** edge triggered storage element
- Common examples of latches:
S-R latch, \bar{S} - \bar{R} latch, D latch (= gated D latch)
- Common examples of flip-flops (FF):
D-FF, D-FF with enable, Scan-FF, JK-FF, T-FF

12 of 29

S-R Latch

X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0

■ S-R (Set-Reset) latch with NOR

- similar to inverter pair, with capability to force output to “0” (Reset=1) or “1” (Set=1)

Inputs		Outputs		
S	R	Q	QN	
0	0	last Q	last QN	(hold)
0	1	0	1	(reset)
1	0	1	0	(set)
1	1	0	0	(forbidden)

13 of 29

S-R Latch Operation

X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0

Hold:

Set:

Hold:


Reset:

S(t)	R(t)	Q(t)	Q(t+ε)	QN(t+ε)
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	Still to analyze	
1	1	1	Still to analyze	

14 of 29

S-R Latch Operation

 - Typical operation of an S-R Latch
- (a) "normal" inputs




Inputs		Outputs		
S	R	Q	QN	
0	0	last Q	last QN	(hold)
0	1	0	1	(reset)
1	0	1	0	(set)
1	1	0	0	(forbidden)


15 of 29

S-R Latch Operation

 - Typical operation of an S-R Latch
- (a) "normal" inputs (b) S and R asserted simultaneously



Inputs		Outputs		
S	R	Q	QN	
0	0	last Q	last QN	(hold)
0	1	0	1	(reset)
1	0	1	0	(set)
1	1	0	0	(forbidden)

 


Both Q and QN are "0" simultaneously

16 of 29


S-R Latch Operation

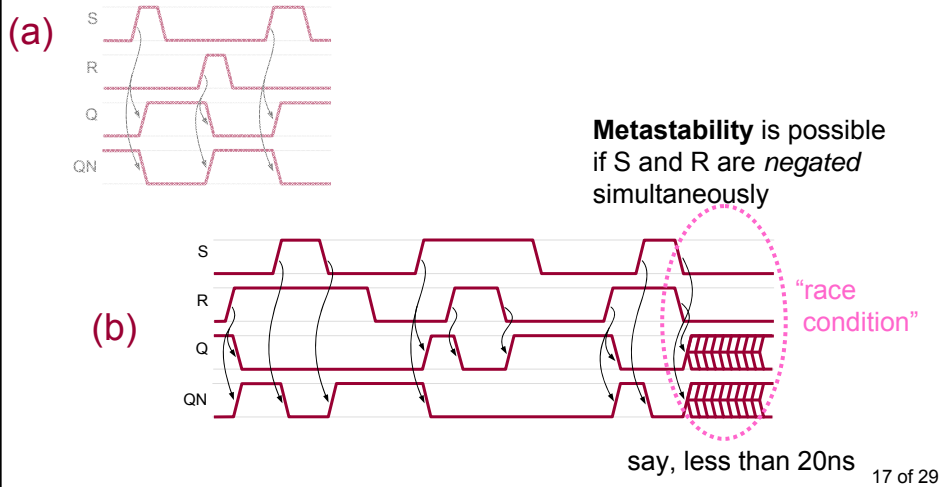- Typical operation of an S-R Latch
- (a) "normal" inputs (b) S and R asserted simultaneously




Improper S-R Latch Operation

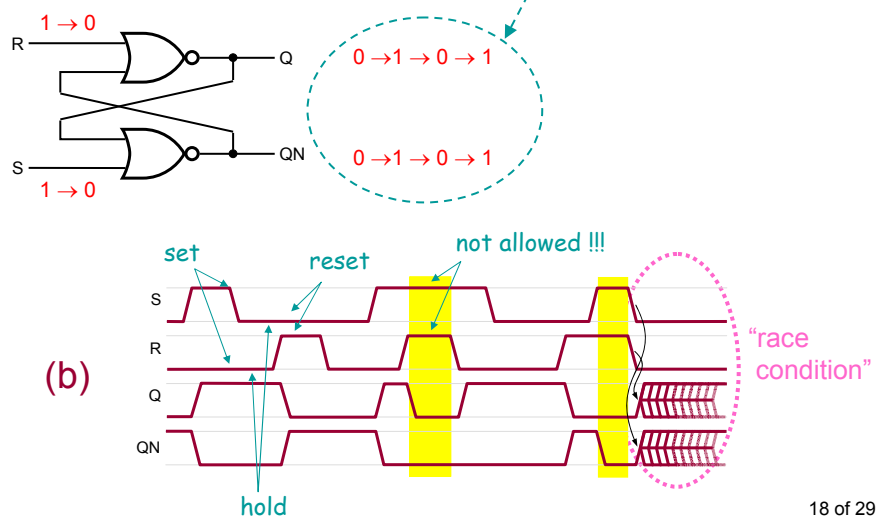- Metastability may occur if S and R are negated simultaneously: the circuit starts to oscillate



S-R Latch Timing Parameters

 - **Propagation delay (t_p)** for an input transition to produce an output
- **Minimum pulse width (t_{pw})** needed for deterministic transitions




- **Recovery time (t_{rec})** = minimum delay between negating S and R for them *not* to be considered simultaneous
- t_{rec} and t_{pw} are related: both measure how long it takes for the latch feedback loop to stabilize
- Violations of t_{pw} and t_{rec} cause *metastability*


19 of 29

R-S Latch Analysis

- Break the feedback path

 


Inputs			Output	
S(t)	R(t)	Q(t)	Q(t+Δ)	
0	0	0	0	(hold)
0	0	1	1	(hold)
0	1	0	0	(reset)
0	1	1	0	(reset)
1	0	0	1	(set)
1	0	1	1	(set)
1	1	0	x	(not allowed)
1	1	1	x	(not allowed)

 

- Next state equation, a.k.a. *characteristic equation*:


$$Q(t+\Delta) = S(t) + R'(t) \cdot Q(t) \quad \Leftrightarrow \quad Q^+ = Q^* = S + R' \cdot Q$$

Theoretical R-S Latch Behavior

 


State diagram

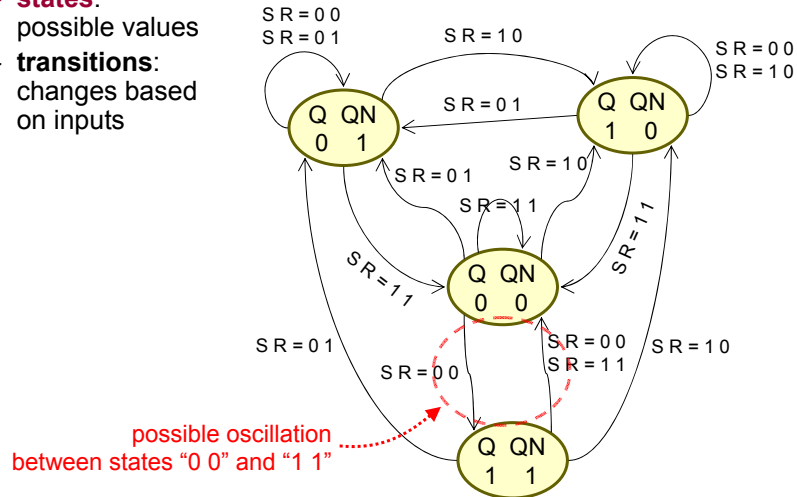- **states:**
possible values
- **transitions:**
changes based on inputs




21 of 29

Observed R-S Latch Behavior

 

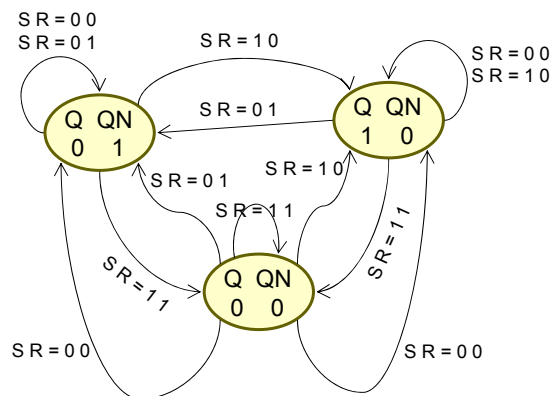- Very difficult to observe R-S latch in the 1-1 state
 - one of R or S usually changes first
 - Ambiguously returns to state 0-1 or 1-0
 - a so-called "race condition"
 - or non-deterministic transition
- metastability





22 of 29

\bar{S} - \bar{R} Latch using NAND gates

- Used more than S-R latch with NOR

  ... because NAND gates are preferred over NOR gates



Inputs		Outputs	
S_L	R_L	Q	QN
0	0	1	1
0	1	1	0
1	0	0	1
1	1	last Q	last QN



- Timing and metastability similar as for S-R

- Next state equation (characteristic equation):

$$Q(t+\Delta) = S'(t) + R(t) \cdot Q(t) \Leftrightarrow Q^+ = Q^* = S' + R \cdot Q$$

Bistable Application: Switch Debouncing

  - Mitigating oscillations in mechanical switches when the wiper makes contact with the terminal





- Problem if the switch is used for counting the number of pushes



Wakerly, Section 8.2.3

Switch Debouncer Wakerly, Section 8.2.3

- No debouncing:

  

- Using a bistable for debouncing:

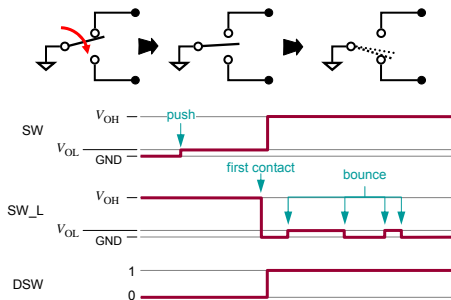 



- SW trying to maintain 0 when the push starts but the first contact with SW_L moves it to 1. After say 30 ns, the switch changes, DSW=1

... see the next slide for details



25 of 29

Using a Bistable for Debouncing

 
 
- Before the button is pushed, the top contact holds SW at 0 V and top inverter produces "1" on SW_L



  
- When the button is pushed and contact is broken, feedback in the bistable holds SW at V_{OL} , i.e., logic "0"



  - When the wiper hits the bottom contact, SW_L is forced to logic "0" and the output of the top inverter also becomes "0"



 
- After this, feedback in the bistable maintains the logic "0" on SW even if the wiper bounces off the bottom contact



26 of 29

Using an S-R Latch for Debouncing


 
- The pull-up resistors avoid the momentarily *shorting* of the gate outputs, when the output of the top inverter is still HIGH and the SW_L becomes connected to the ground



27 of 29

S-R Latch with Enable

  - Sensitive to S/R inputs only when an enabling input **C** is asserted ("C" stands for "clock")



Inputs			Outputs	
S	R	C	Q	QN
0	0	1	last Q	last QN
0	1	1	0	1
1	0	1	1	0
1	1	1	1	1
x	x	0	last Q	last QN

28 of 29

S-R Latch with Enable

- Typical operation
- If both S and R are “1” when the enabling input C is turned from “1” to “0”, the circuit behaves like an S-R latch and the output can become metastable

