



14:332:231 DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University
Electrical & Computer Engineering
Fall 2013


Lecture #16: D Latch ; Flip-Flops

D Latch

  - “Data” latch: single input “D”, plus enable input “C”
- The D Latch eliminates the S=R=1 problem of the SR latch
- However, violations of setup and hold time still cause metastability ...



Inputs		Outputs	
C	D	Q	QN
1	0	0	1
1	1	1	0
0	x	last Q	last QN

 


Characteristic equation:

$$Q^* = C' \cdot Q + C \cdot D$$

2 of 23

D Latch Operation

 
- Functional behavior of a D latch for various inputs:
 - When the enable input C is asserted, the Q output follows the D input
 - The latch is said to be “open” and the path from D input to Q output is “transparent” → *transparent latch*
 - When enable (C) is asserted, the latch acts like a combinational circuit!



3 of 23

D Latch Timing Parameters

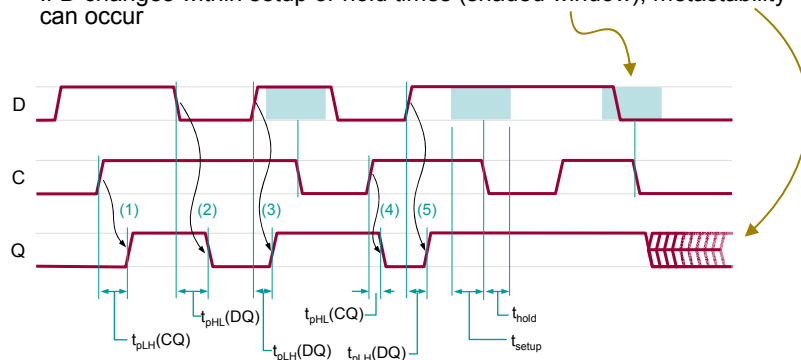- Propagation delay (from C or D to output Q)
- Setup time (D before C falling/rising edge)
- Hold time (D after C falling/rising edge)
 - If D changes within setup or hold times (shaded window), metastability can occur



(1) & (4) — Latch initially closed and when C asserted, Q changes
 (2), (3) & (5) — Latch already opened, so Q transparently follows D

4 of 23


Latch Issues

- Latches can cause serious timing problems (races) in sequential circuits
 - Due to the fact that a latch is “transparent”:
 - $D = Q$ while the clock $C = 1$
 - *Advantage*: input changes can be seen immediately at output
 - *Disadvantage*: output changes every time input changes (while $C = 1$)
 - Desired behavior for a memory device:
 - stored value changes only at discrete time instants, determined by rising or falling edges of *clock* signal
- The timing problems can be avoided by using “Flip-Flops”

5 of 23

The Latch Timing Problem (cont'd)

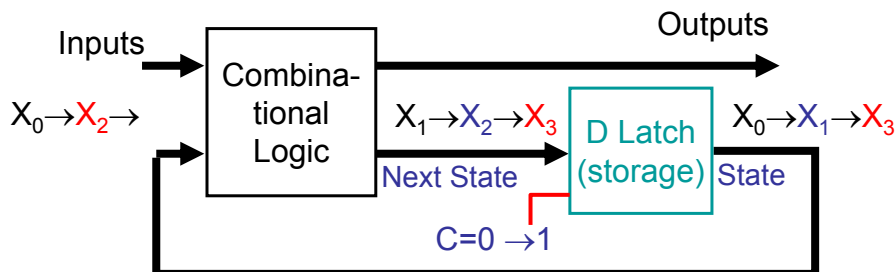- Similar timing problems in the sequential circuits:
 - Recall that an enabled latch acts like a combinational circuit
 - Hence, we possibly have two cascaded combinational circuits feeding each other, generating oscillations and unstable transient behavior






- Need for circuits that change state **only once per clock cycle**:
 - $C=1$:
 - Now the current state becomes X_1 and a new state is generated by the combinational logic circuit: X_2 .
 - However, if $C=1$, the new “next state” X_2 will create a new current state $X_2!$, etc...

6 of 23

Use Flip-flops to Solve the Timing Problem

   - A solution to the latch timing problem is to break the closed path from In to Out within the storage element




7 of 23


Clock Signals

- Clocks are regular periodic signals used to specify state changes
- Very important for sequential circuits
 - State variables change state at the clock edge

Active high:

 


Active low:

 

8 of 23

Flip-flops

 - Flip-flops change state only on the edge of a clock (CLK) pulse (either rising or falling edge)
 - Symbolized by the *dynamic input indicator* \triangleright
- Clock is *active high* \rightarrow then the state changes on the *rising* (positive) edge
- Clock is *active low* \rightarrow then the state changes on the *falling* (negative) edge





9 of 23

The D Flip-flop: The Principle

- Positive-edge triggered D flip-flop
- Inputs sampled on rising edge; outputs change after rising edge

Inputs		Outputs	
D	CLK	Q	Q \bar{N}
0		0	1
1		1	0
x	0	last Q	last Q \bar{N}
x	1	last Q	last Q \bar{N}


Next-state equation: $Q^* = D$

  

10 of 23

The D Flip-flop: Implementation

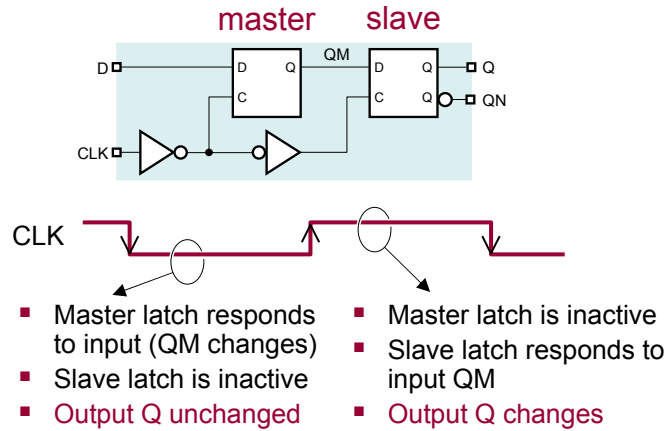- Consists of two clocked D latches in series with the clock on the second latch inverted




11 of 23

The D Flip-flop: Implementation

- Positive-edge triggered D flip-flop:
 - Output changes at positive clock edge

Recall D latch table:



Inputs		Outputs	
C	D	Q	QN
(enabled) 1	0	0	1
(enabled) 1	1	1	0
(hold) 0	x	last Q	last QN

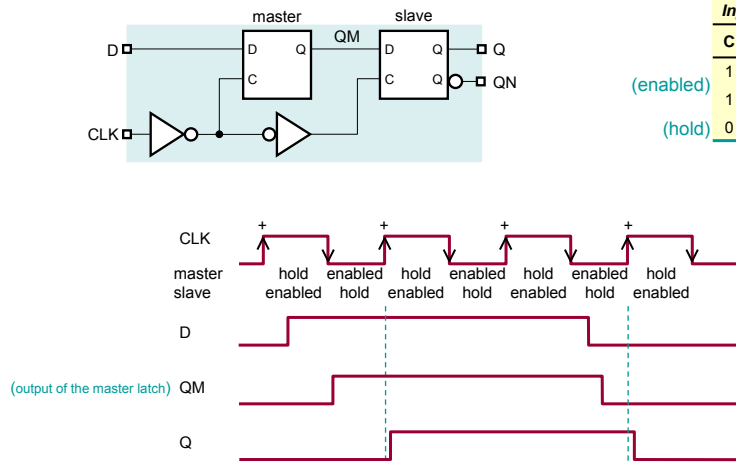

12 of 23

Edge-triggered D Flip-flop Behavior

  - Master latch output QM changes only when CLK is "0"
- When CLK → "1", the current QM value is transferred to Q



Inputs		Outputs	
D	CLK	Q	QN
0	1	0	1
1	1	1	0
x	0	last Q	last QN
x	1	last Q	last QN

13 of 23

Flip-flop Timing Constraints


Proper operation requires strict timing rules:

- **Minimum clock pulse width:** t_{pw} (t_{pwH} , t_{pwL})
- **Set-up time** (t_{setup}):
minimum time that the input signal must be present **prior to a clock edge**
- **Hold time** (t_{hold}): minimum time the input must be kept after the clock edge

14 of 23

D Flip-flop Timing Parameters


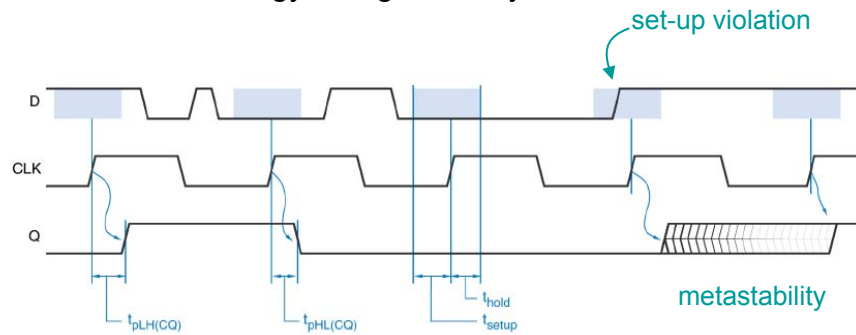
- Propagation delay (from CLK)
- Setup time (D before CLK)
- Hold time (D after CLK)
- Shaded window duration is $t_{\text{setup}} + t_{\text{hold}}$ — values depend on the technology and gate delays



15 of 23

Other D Flip-flop Variations

  - Negative-edge triggered D flip-flop
 - Simply inverts the clock input — active low
 - Action takes place on the falling edge of CLK_L




Inputs		Outputs	
D	CLK_L	Q	Q \bar{N}
0		0	1
1		1	0
x	0	last Q	last Q \bar{N}
x	1	last Q	last Q \bar{N}

16 of 23

D Flip-flop w/ Asynchronous Inputs

 - with **Preset** (PR) and **Clear** (CLR), similar to set/reset of S-R latch
 - Used to force the flip-flop to a particular state independent of CLK & D
 - Suitable for initialization and testing purposes, e.g., to initialize a counter
- Positive-edge-triggered




- Placing a "0" on CLR_L forces the state Q = 0
- If CLR_L = 1, no effect on NAND gates
- Similarly, PR_L = 0 forces the state Q = 1, and PR_L = 1 has no effect

17 of 23


Clock Enable Positive-edge-triggered D Flip-flop

 - Flip-flops sometimes include additional logic: Clock enable (EN or CE)
- At clock edge, holds the last value stored, rather than load a new value
- A 2-input multiplexer controls the input value of the internal D flip-flop



Inputs			Outputs	
D	EN	CLK	Q	QN
0	1		0	1
1	1		1	0
x	0		last Q	last QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN

 - If EN is asserted, the external input D is selected
- If EN is negated, the flip-flop's current output is used



18 of 23



Sections not covered & not required...

- Wakerly, Section 7.2.7
“Scan Flip-flop”
- Wakerly, Section 7.2.8
“Master/slave S-R Flip-flop”
- Wakerly, Section 7.2.9
“Master/slave J-K Flip-flop”

19 of 23

Edge-triggered J-K Flip-flop

  - Not used much anymore, except in the lab ...



Next-state equation: $Q^* = J \cdot Q' + K' \cdot Q$


Inputs			Outputs	
J	K	CLK	Q	QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN
0	0	\uparrow	last Q	last QN
0	1	\uparrow	0	1
1	0	\uparrow	1	0
1	1	\uparrow	last QN	last Q

20 of 23

Functional Behavior of a Positive-edge-triggered J-K Flip-flop

- The commercial version is a TTL positive-edge-triggered J-K flip-flop 74x109


Inputs			Outputs	
J	K	CLK	Q	QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN
0	0	\downarrow	last Q	last QN
0	1	\downarrow	0	1
1	0	\downarrow	1	0
1	1	\downarrow	last QN	last Q

 


21 of 23

T (toggle) Flip-flop

 
- Changes state at every clock tick
 - Signal on the Q output has frequency = $\frac{1}{2} T$
- Used in counters and frequency dividers
- Can be constructed from D or J-K flip-flops



D flip-flop:

 

J-K flip-flop:


 


Next-state equation: $Q^* = Q'$


22 of 23

T (toggle) Flip-flop with Enable

  
- Flip-flop toggled only when enabled
 - Important for counters
- t_{setup} and t_{hold} must be satisfied w.r.t. T and EN



T flip-flop with enable: D

 

J-K flip-flop

 

Next-state equation: $Q^* = Q \oplus EN$