

# 14:332:231 DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University  
Electrical & Computer Engineering  
Fall 2013

Lecture #18: State Machine Design and Synthesis

## State Machine Design and Synthesis

The creative part (“art”),  
like writing a program


“Turning the crank”,  
like a compiler does

- The flowchart is in *inverse sequence* (compared to analysis). The state/output comes the first and the drawing of the logic diagram comes the last:

state/output table → transition table  
→ transition equation → characteristic equation  
→ excitation equation → logic diagram

## Clocked Synchronous FSM Structure

 - Example: Design a combination lock with two inputs, X1 and X2.  
Open for the sequence X1, X2, X2 (one input per clock)
- Success scenario:



- But there are many potential failure scenarios that need to be considered ...

3 of 25

## Clocked Synchronous FSM Structure

- Example: Design a combination lock with two inputs, X1 and X2.  
Open for the sequence X1, X2, X2 (one input per clock)

State		inputs				Output
		X1	X2	X1	X2	
Meaning	Name	00	01	10	11	UNLOCK
Start	A	A	A	B	A	0
Got X1	B	A	C	A	A	0
Got X1, X2	C	A	D	A	A	0
Got X1, X2, X2	D	A	A	B	A	1

A blue dashed box highlights the next state entries for states A, B, C, and D. An arrow labeled "next state" points from the '11' input column to the 'A' entry in the 'Got X1' row.

- Specification ambiguities are resolved in the state table

4 of 25

# State Assignment

- Can minimize the number of states but hardly anyone bothers anymore
- Need to assign binary-variable combinations to states
  - Minimum number of variables for  $n$  states is  $\lceil \log_2 n \rceil$
  - Using *more than minimum* number may be advantageous in some situations, e.g., one variable per state  
(“one-hot”: one-out-of- $n$  pattern)
  - Example: 4 states  $\rightarrow$  2 state variables (Q1, Q2)

A = 00  
B = 01  
C = 10  
D = 11

Up to this point is the “art” part of FSM design; the rest is just “turning the crank” part

5 of 25

# Transition Table


- Substitute state-variable combinations for symbolic state names in the state table

State		X1 X2				Output
Meaning	Q1 Q2	00	01	10	11	UNLOCK
Start	00	00	00	01	00	0
Got X1	01	00	10	00	00	0
Got X1, X2	10	00	11	00	00	0
Got X1, X2, X3	11	00	00	01	00	1
		Q1* Q2*				

6 of 25
 
## Transition Equations; Circuit


- Transition table specifies each state variable ( $Q1^*$ ,  $Q2^*$ ) as a combinational logic function of  $Q1$ ,  $Q2$ ,  $X1$ ,  $X2$ 
  - Find a realization of each function by your favorite means—ad hoc, minimal sum-of-products, etc.
- Build the circuit



7 of 25

## A Complete Design Example

 - PROBLEM:** Design a machine with inputs  $A$  and  $B$  and output  $Z$  that is “1” if any is true:
  - $A$  had the same value at the *two previous* ticks
- OR:**  $B$  has been “1” since *the last time* the above was true



8 of 25

# A Complete Design Example

- PROBLEM: Design a machine with inputs A and B and output Z that is “1” if any is true:
  - A had the same value at the *two previous* ticks
- OR: – B has been “1” since *the last time* the above was true

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	?	?	?	?	0
S*						

State with symbolic name “A0” means:

Got A=0 on the previous tick, A≠0 on the tick before that, and B≠1 at some time since the previous pair of equal A inputs

9 of 25

# A Complete Design Example

- PROBLEM: Design a machine with inputs A and B and output Z that is “1” if any is true:
  - A had the same value at the *two previous* ticks
- OR: – B has been “1” since *the last time* the above was true

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	?	?	?	?	0
S*						



Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	OK	OK	A1	A1	0
Got a 1 on A	A1					0
Two equal A inputs	OK	?	?	?	?	1
S*						

State “OK” means:

Got a pair of equal A inputs (0,0 or 1,1) on the previous two ticks.

Remains in “OK” state as long as A remains constant or B=1.

But, how to know if A “remained constant” ? → need to split “OK” state


10 of 25

# A Complete Design Example

- PROBLEM: Design a machine with inputs A and B and output Z that is "1" if any is true:
  - A had the same value at the *two previous* ticks
- OR: B has been "1" since *the last time* the above was true
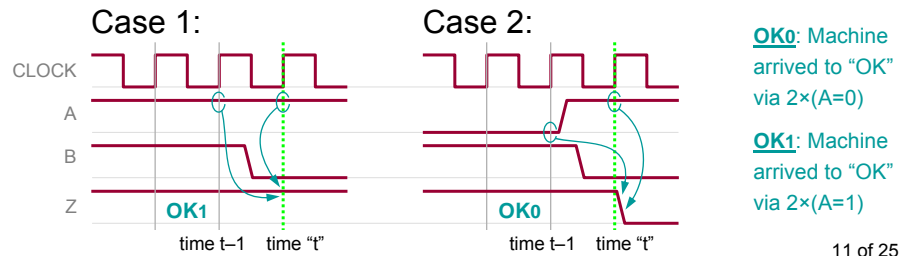
## Why we need to split the state "OK" into OK0 and OK1:

- If we don't know what was the value of A before time "t", then when B≠1, we cannot know if A "remained constant" (Case 1) or not (Case 2)



# A Complete Design Example

- PROBLEM: Design a machine with inputs A and B and output Z that is "1" if any is true:
  - A had the same value at the *two previous* ticks
- OR: B has been "1" since *the last time* the above was true

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	OK0	OK0	A1	A1	0
Got a 1 on A	A1	A0	A0	OK1	OK1	0
Two equal, A=0 last	OK0	OK0	OK0	OK1	A1	1
Two equal, A=1 last	OK1	A0	OK0	OK1	OK1	1
		S*				

Machine arrived to "OK" via 2×(A=0)

Machine arrived to "OK" via 2×(A=1)


- We achieved "closure" of the state table, which now describes a *finite*-state machine

# Timing Diagram for Example FSM

- Output Z is "1" if any is true:
  - A had the same value at the *two previous ticks*
- OR:** B has been "1" since *the last time* the above was true

S	A B				Z
	00	01	11	10	
INIT	A0	A0	A1	A1	0
A0	OK0	OK0	A1	A1	0
A1	A0	A0	OK1	OK1	0
OK0	OK0	OK0	OK1	A1	1
OK1	A0	OK0	OK1	OK1	1

S\*

 


illustrates why OK0 vs. OK1 needed

13 of 25
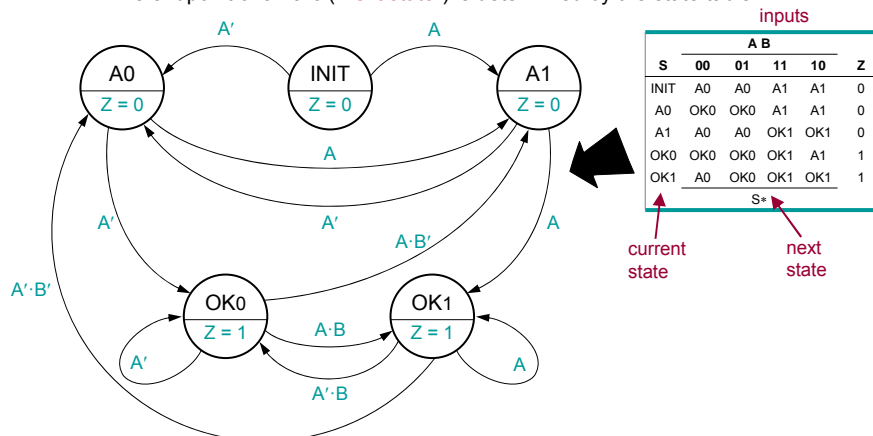
# State Diagram

- State Diagram is drawn from the state/output table:
  - First draw ovals for all states
  - Second, for each state ("current state") draw outgoing arcs for different inputs
    - The endpoint of an arc ("next state") is determined by the state table:



14 of 25

## State Assignment

- Determine how many binary variables to represent the states in the state table
  - For  $s$  states we need  $\lceil \log_2 s \rceil$  binary variables
- **Coded state** = binary combination assigned to a particular state
- In our example:
  - five states  $\rightarrow \lceil \log_2 5 \rceil = 3$
  - $2^3 = 8 \rightarrow$  three unused binary combinations (a.k.a. unused coded states)

15 of 25

## State Assignment

- There are  $\binom{8}{5} = 6,720$  different state assignments of 5 states to 8 possible states (3 binary variables)
  - And there are many more using 4 or more binary variables
- Simplest is *counting order*, but may not lead to simplest excitation & output equations, nor the simplest logic circuit

Coded State Assignment	
State Name	Simplest Q1-Q3
INIT	000
A0	001
A1	010
OK0	011
OK1	100

16 of 25



## Heuristics for "Best" State Assignment

- Choose an initial coded state into which the machine can be easily forced at reset
- Minimize the number of state variables that change on each transition
- Maximize the number of variables that don't change in a group of "related" states
- Exploit symmetries in problem-spec / state-table
- Decompose the set of variables into individual bits, where each bit has a well-defined meaning w.r.t. input effects or output behavior of the machine
- Etc. → see Wakerly, 4<sup>th</sup> edition, page 561

17 of 25

## State Assignment Examples

- Here are a few "obvious" or "interesting" assignments
  - *Decomposed*:
    - Initial state is "000", which is easy to force to, e.g., applying RESET signal to flop-flops' CLR inputs
    - For remaining four states, Q1 used to indicate if the machine is in INIT
    - When Q1=1, Q2 and Q3 used to distinguish among the four non-INIT states
  - *One-hot* uses one bit per state (one-out-of-5 pattern: 5 bits instead of minimum 3)
    - Advantage: leads to simple excitation equations || Disadvantage: requires more flip-flops
  - *Almost One-hot* — uses "no-hot" combination "0000" for the initial state

State Name	Coded State Assignment			
	Simplest Q1-Q3	Decomposed Q1-Q3	One-hot Q1-Q5	Almost One-hot Q1-Q5
INIT	000	000	00001	0000
A0	001	100	00010	0001
A1	010	101	00100	0010
OK0	011	110	01000	0100
OK1	100	111	10000	1000

18 of 25

## Dealing with Unused States

- Minimum risk:  
 Assuming that the machine may somehow get into one of the unused (or “illegal”) states, all unused states automatically go to the “initial” state  
 (we will *first* use this design for our example)
- Minimal cost:  
 Assuming that the machine will never enter an unused state, all unused states are labeled with “d” (don’t-care) and are used if the minimization requires it  
 (will see this design later)

19 of 25

## Transition/Output Table

- For *transition table*, simple textual substitution
- Assuming “decomposed” state assignment:

S	A B				Z
	00	01	11	10	
INIT	A0	A0	A1	A1	0
A0	OK0	OK0	A1	A1	0
A1	A0	A0	OK1	OK1	0
OK0	OK0	OK0	OK1	A1	1
OK1	A0	OK0	OK1	OK1	1
S*					

Q1 Q2 Q3	A B				Z
	00	01	11	10	
000	100	100	101	101	0
100	110	110	101	101	0
101	100	100	111	111	0
110	110	110	111	101	1
111	100	110	111	111	1
Q1* Q2* Q3*					


state/output table

transition/output table

20 of 25
 
# Excitation Table ( "decomposed" state assignment )


- Assuming D flip-flops (characteristic equation  $Q^* = D$ ), *excitation table* is identical to transition table,  $D = Q^*$



21 of 25
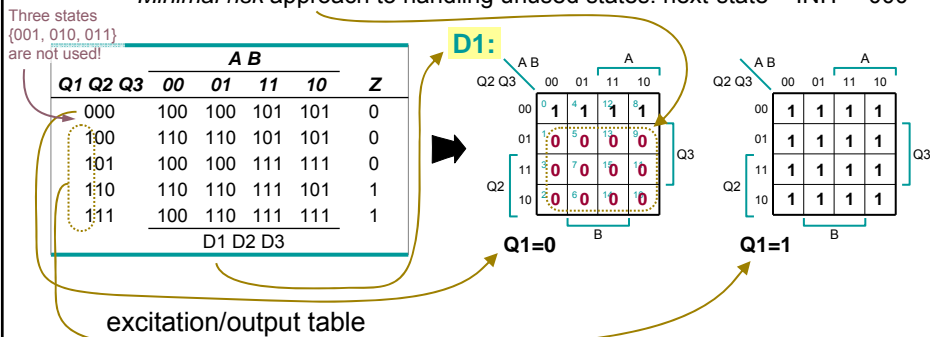
# Excitation Table as Truth Table


- Excitation table as *truth table* for three combinational logic functions (D1, D2, D3) and five variables (A, B, Q1, Q2, Q3)
- Developing excitation equations using a *5-variable Karnaugh map* [recall **Lecture #7**]
- But, excitation table is not quite a truth table—doesn't specify functional values for *all* input combinations (i.e., unused states)
  - Minimal risk* approach to handling unused states: next-state = INIT = 000



22 of 25
 
# Developing Excitation Equations

- Excitation maps for **D1**, **D2**, and **D3** assuming that unused states have "0 0 0" as the *next-state*




- Flip-flop excitation inputs:  
 $D1 = Q1 + Q2' \cdot Q3'$   
 $D2 = Q1 \cdot Q3' \cdot A' + Q1 \cdot Q3 \cdot A + Q1 \cdot Q2 \cdot B$   
 $D3 = Q1 \cdot A + Q2' \cdot Q3' \cdot A$   
 $Z = Q1 \cdot Q2 \cdot Q3' + Q1 \cdot Q2 \cdot Q3 = Q1 \cdot Q2$

23 of 25
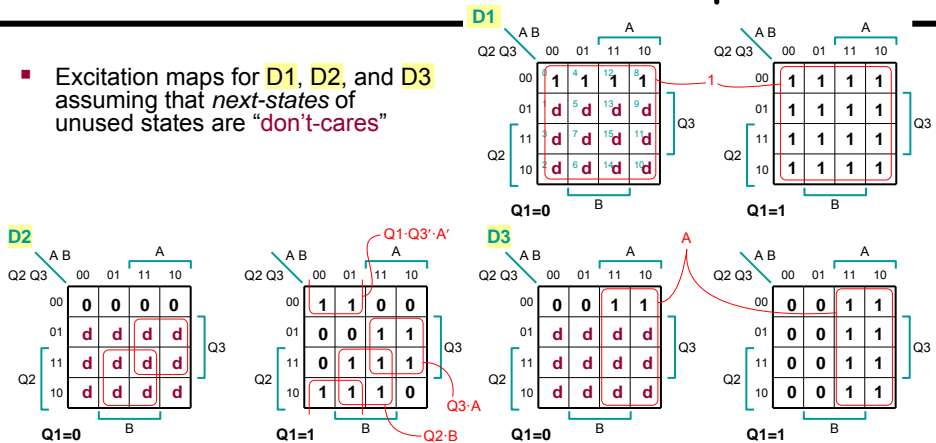
# Minimal Cost Excitation Equations

- Excitation maps for **D1**, **D2**, and **D3** assuming that *next-states* of unused states are "don't-cares"




- Flip-flop excitation inputs are now simpler ("minimal cost"):  
 $D1 = 1$   
 $D2 = Q1 \cdot Q3' \cdot A' + Q3 \cdot A + Q2 \cdot B$   
 $D3 = A$   
 $Z = Q2$

draw the circuit ...

24 of 25
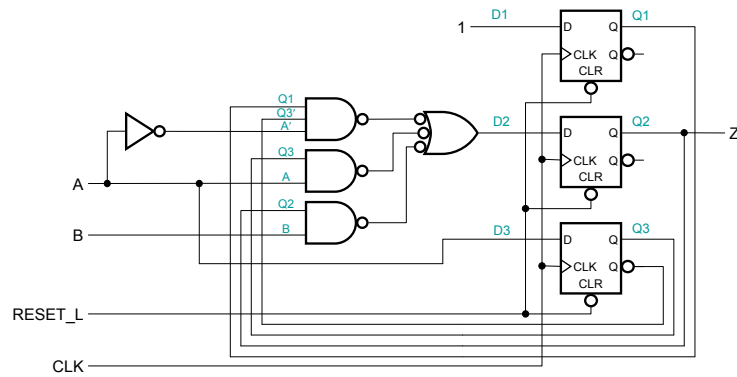
# Minimal Cost Circuit

- Logic diagram for the excitation maps using “don't-cares” as next states of unused states



25 of 25