

14:332:231

DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University
Electrical & Computer Engineering
Fall 2013

Lecture #19: Designing State Machines Using State Diagrams


Design Steps Using State Diagrams

- Identify the inputs and outputs
- Identify the states (by their symbolic names)
- Draw the state diagram
- Analyze the state diagram for ambiguities
 - If ambiguities found, go back and modify the diagram and analyze again
 - **iterative process**, as the problem and solution become clearer in the designer's mind
- Derive the transition list
- Synthesize the circuit from the transition list

2 of 22

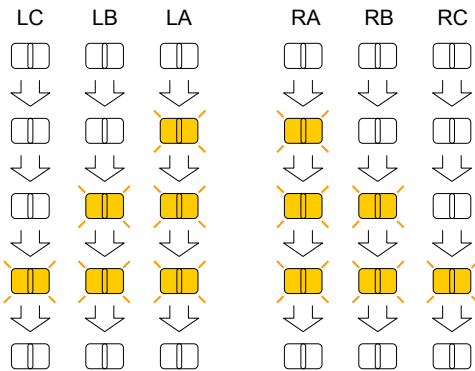Example State Machine

- Controlling the tail lights of a 1965 Ford Thunderbird
- Flashing sequence for: left turn and right turn



LC LB LA RA RB RC

Hazard (HAZ) lights:
All 6 lights are flashing

3 of 22

Identifying Inputs and Outputs

- Left-turn signal lever (**LEFT**)
- Right-turn signal lever (**RIGHT**)
- Hazard lights push-button (**HAZ**)
- OUTPUTS: LA, LB, C, RA, RB, RC



4 of 22

Identifying States

and their Symbolic Names

LC	LB	LA	RA	RB	RC	
						← IDLE
						← L1
						← L2
						← L3
						← R1
						← R2
						← R3
						← LR3 (hazard lights)

Initial State Diagram

- Moore machine: output depends only on current state
- Label "1" on a transition arc indicates that all input is ignored and the machine transitions to the next state upon completion of current-state/output computation


Output Table

State	LC	LB	LA	RA	RB	RC
IDLE	0	0	0	0	0	0
L1	0	0	1	0	0	0
L2	0	1	1	0	0	0
L3	1	1	1	0	0	0
R1	0	0	0	1	0	0
R2	0	0	0	1	1	0
R3	0	0	0	1	1	1
LR3	1	1	1	1	1	1

← Hazard


Output Equations
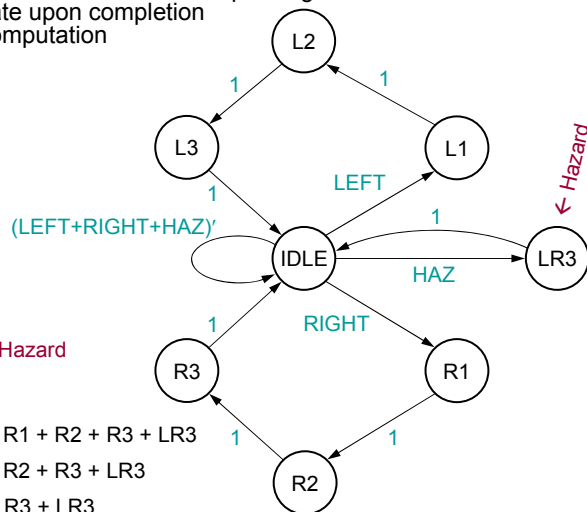
$$\begin{aligned}
 LA &= L1 + L2 + L3 + LR3 & RA &= R1 + R2 + R3 + LR3 \\
 LB &= L2 + L3 + LR3 & RB &= R2 + R3 + LR3 \\
 LC &= L3 + LR3 & RC &= R3 + LR3
 \end{aligned}$$



Corrected State Diagram

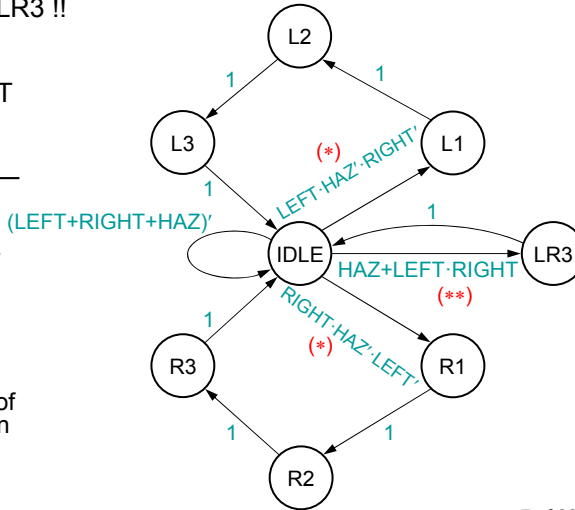
- Problem:** doesn't properly handle multiple inputs asserted simultaneously e.g., if in IDLE both LEFT and HAZ are asserted the machine goes to 2 states: L1 and LR3 !!
- Corrections:**
 - (*) give HAZ priority;
 - (**) treat concurrent LEFT and RIGHT as HAZ
- The corrected state diagram—** transition expressions on arcs are:
 - mutually exclusive:** for each state, the product of any pair of outgoing transition expressions is "0"
 - all-inclusive:** for each state, the sum of transition expressions on all outgoing arcs is "1"



7 of 22

Enhanced State Diagram

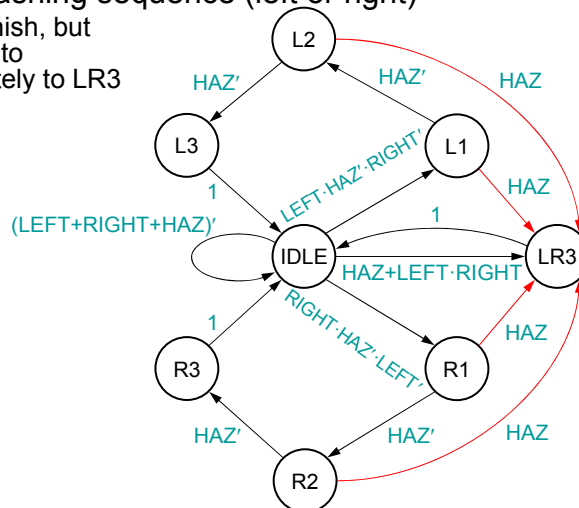- Problem:** What if HAZ is activated while the machine cycles through a flashing sequence (left or right)
 - The cycle would finish, but a better solution is to transition immediately to LR3



8 of 22


Ambiguity in State Diagram

- In a properly constructed state diagram, each input combination is covered exactly once by an expression of an outgoing arc
- Ambiguous: double-covered or uncovered
- Some input combinations are covered by more than one expressions (**double-covered**)
 - Given such an input combination, there are two or more next-state-transitions to follow
 - **Mutual exclusion**: AND of any pair of expressions should be “0”
- Some input combinations are not covered by any expressions (**uncovered**)
 - Given such an input combination, there are no any next-state-transitions to follow
 - **All-inclusion**: OR of all expressions should be “1”


9 of 22

State Diagram Ambiguities - Example

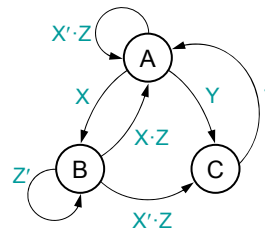- Example state diagram:
 - States: A, B, C
 - Inputs: X, Y, Z
- Karnaugh-like maps:
 - Consider each state separately
 - Draw a different K-map for each state
 - Each cell represents a unique combination of inputs
 - For all outgoing transitions fill in the corresponding cells with next state
- Each cell should have one and only one entry:
 - An *empty* cell (“uncovered”) indicates the **All-inclusion rule** has been violated
 - *More than one entry* indicates the **Mutual-exclusion rule** has been violated




Current state:

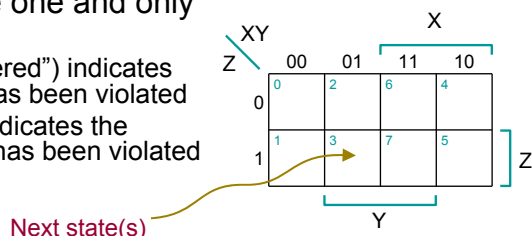


10 of 22

State Diagram Ambiguities - Example

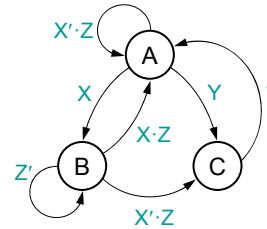- **in state A:**
 - for input $X=1$, transition to next-state B
→ fill in corresponding K-map cells with “B”
 - for input $Y=1$, transition to C
→ fill in corresponding K-map cells with “C”
 - for input $X=0, Z=1$, transition to A
→ fill in corresponding K-map cells with “A”



Current state A:

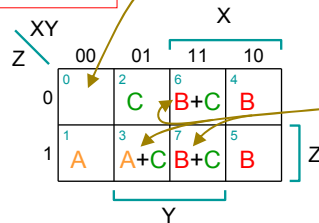


- Empty cell (“uncovered”):
 - All-inclusion rule violated
- Multiple entries (“doubly covered”):
 - Mutual-exclusion rule violated
- State A not unambiguously specified !!


11 of 22

State Diagram Ambiguities - Example

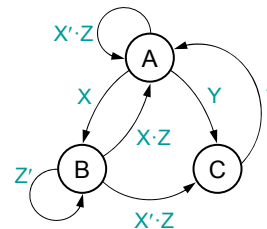- **in state B:**
 - for input $Z=0$, transition to next-state B
→ fill in corresponding K-map cells with “B”
 - for input $X=1, Z=1$, transition to A
→ fill in corresponding K-map cells with “A”
 - for input $X=0, Z=1$, transition to C
→ fill in corresponding K-map cells with “C”



Current state B:

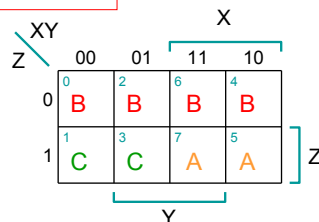

- No ambiguities — each cell has one and only one entry
- State B is unambiguously specified !!
- **NOTE:** State C is unambiguously specified because of the unconditional transition to A (indicated by “1” on the outgoing arc)

12 of 22

State Assignment

(Back to the T-bird lights example...)

- For 8 states, need 3 flip-flops
- Initial (IDLE) state coded as “000” for easy reset
- State variable Q2 used to distinguish “left” vs. “right”
- State variables Q1 and Q0 used to “count” in Gray-code sequence: IDLE→L1→L2→L3→IDLE
 - Minimizes the number of state-variable changes per transition
- The remaining binary combination “100” used for the LR3 state


State Assignment

State	Q2	Q1	Q0
IDLE	0	0	0
L1	0	0	1
L2	0	1	1
L3	0	1	0
R1	1	0	1
R2	1	1	1
R3	1	1	0
LR3	1	0	0

13 of 22

Listing Next State Transitions

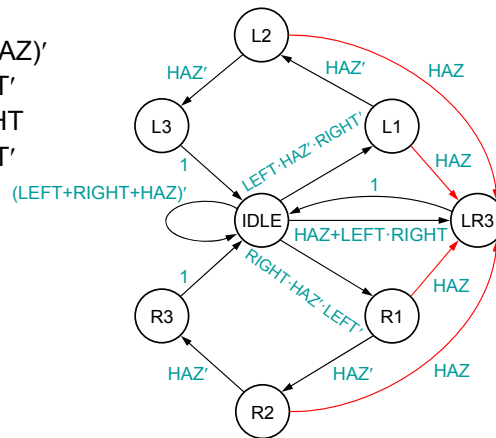- From state IDLE:
 - Input: $(LEFT+RIGHT+HAZ)'$
 - Input: $LEFT \cdot HAZ' \cdot RIGHT'$
 - Input: $HAZ + LEFT \cdot RIGHT$
 - Input: $RIGHT \cdot HAZ' \cdot LEFT'$
- From state L1:
 - Input: HAZ
 - Input: HAZ'
- From state L2:
 - Input: HAZ
 - Input: HAZ'
- From state L3:
 - Input: 1 (state completion transition)
- ...



14 of 22

Transition List

- Similar to a *transition table*, but transitions in the state diagram are specified by expressions, not by an extensive tabulation of next states

Current State				Transition Expression	Next State				
S	Q2	Q1	Q0		S*	Q2*	Q1*	Q0*	
Outgoing Transitions	IDLE	0	0	0	(LEFT + RIGHT + HAZ)'	IDLE	0	0	0
	IDLE	0	0	0	LEFT · HAZ' · RIGHT'	L1	0	0	1
	IDLE	0	0	0	HAZ + LEFT · RIGHT	LR3	1	0	0
	IDLE	0	0	0	RIGHT · HAZ' · LEFT'	R1	1	0	1
	L1	0	0	1	HAZ'	L2	0	1	1
	L1	0	0	1	HAZ	LR3	1	0	0
	L2	0	1	1	HAZ'	L3	0	1	0
	L2	0	1	1	HAZ	LR3	1	0	0
	L3	0	1	0	1	IDLE	0	0	0
	R1	1	0	1	HAZ'	R2	1	1	1
	R1	1	0	1	HAZ	LR3	1	0	0
	R2	1	1	1	HAZ'	R3	1	1	0
	R2	1	1	1	HAZ	LR3	1	0	0
	R3	1	1	0	1	IDLE	0	0	0
	LR3	1	0	0	1	IDLE	0	0	0

From a transition list, circuit synthesis is just "turning-the-crank," — automated using a CAD tool

15 of 22

Synthesizing Circuit from Transition List

- Transition equation
 - $V^* = \sum_{\text{transition-list rows where } V^*=1} (\text{transition p-term})$
 - A p-term is the product of current state's minterm and the transition expression

- The transition equation for Q2* is the T-bird machine:

$$\begin{aligned}
 Q2^* = & Q2' \cdot Q1' \cdot Q0' \cdot (HAZ + LEFT \cdot RIGHT) \\
 & + Q2' \cdot Q1' \cdot Q0' \cdot (RIGHT \cdot HAZ' \cdot LEFT') \\
 & + Q2' \cdot Q1' \cdot Q0 \cdot (HAZ) \\
 & + Q2' \cdot Q1 \cdot Q0 \cdot (HAZ) \\
 & + Q2 \cdot Q1' \cdot Q0 \cdot (HAZ') \\
 & + Q2 \cdot Q1' \cdot Q0 \cdot (HAZ) \\
 & + Q2 \cdot Q1 \cdot Q0 \cdot (HAZ') \\
 & + Q2 \cdot Q1 \cdot Q0 \cdot (HAZ)
 \end{aligned}$$

- After simplification:


$$\begin{aligned}
 Q2^* &= Q2' \cdot Q1' \cdot Q0' \cdot (HAZ + RIGHT) + Q2' \cdot Q0 \cdot (HAZ) + Q2 \cdot Q0 \\
 Q1^* &= Q0 \cdot HAZ' \\
 Q0^* &= Q2' \cdot Q1' \cdot Q0' \cdot HAZ' \cdot (LEFT \oplus RIGHT) + Q1' \cdot Q0 \cdot HAZ'
 \end{aligned}$$

- Note: These equations are not necessarily minimal

16 of 22

Another State-Machine Design Example

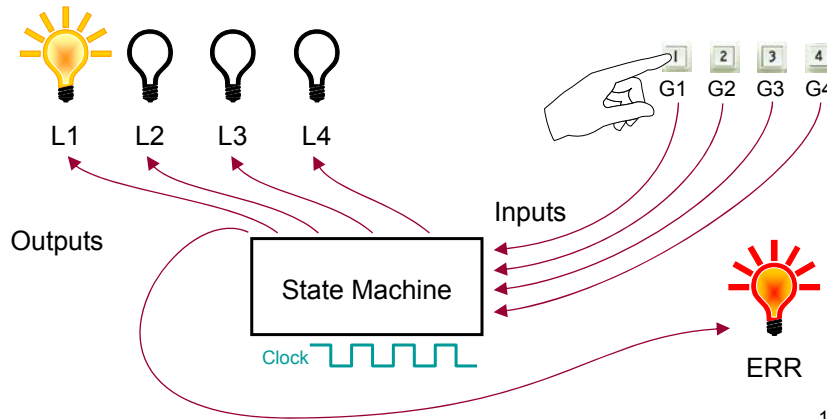
- The Guessing Game
 - 1-out-of-4 lamps lit
 - At each clock tick, the pattern is rotated by one
 - Make a guess by pressing a button G_i :
 - If $G_i = \text{asserted}(L_i)$ play stops
 - If $G_i \neq \text{asserted}(L_i)$ play stops and ERR lamp is lit



17 of 22

State Diagram - First Try

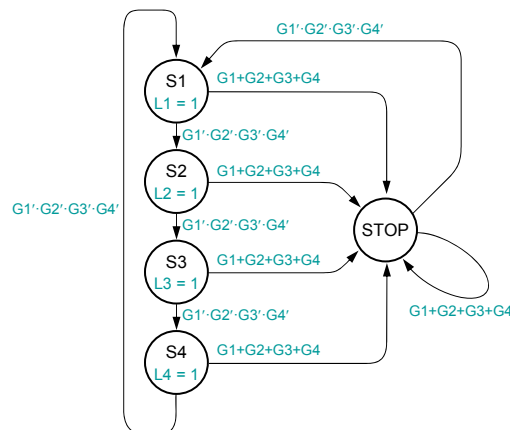
- Machine cycles through states S_1 – S_4 as long as no G_i is asserted
- Goes to STOP when a guess is made
- **PROBLEM:** In STOP, doesn't "remember" if guess was correct, so cannot control ERR lamp
 - Moore machine: output depends on current state only



18 of 22

State Diagram - Corrected

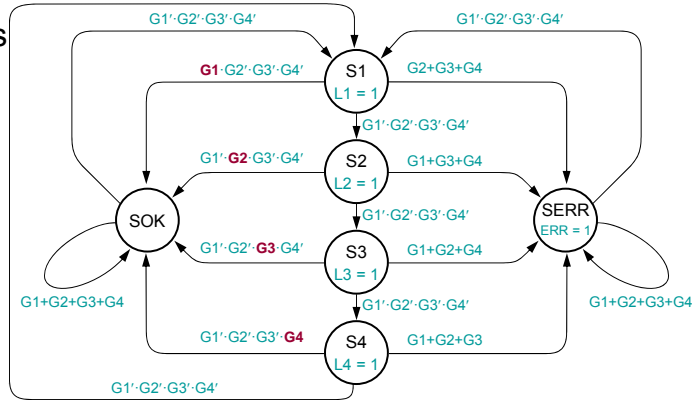- Solution: two “stopped” states, SOK and SERR
 - SOK = correct guess
 - SERR = wrong guess → assert ERR output
- Machine goes to SERR if user presses ≥2 buttons at once or changes guess while in STOP



19 of 22

Transition List for Guessing Game

	Current State				Transition Expression	Next State				Output				
	S	Q2	Q1	Q0		S*	Q2*	Q1*	Q0*	L1	L2	L3	L4	ERR
Outgoing Transitions	S1	0	0	0	G1'G2'G3'G4'	S2	0	0	1	1	0	0	0	0
	S1	0	0	0	G1'G2'G3'G4'	SOK	1	0	0	1	0	0	0	0
	S1	0	0	0	G2+G3+G4	SERR	1	0	1	1	0	0	0	0
	S2	0	0	1	G1'G2'G3'G4'	S3	0	1	1	0	1	0	0	0
	S2	0	0	1	G1'G2'G3'G4'	SOK	1	0	0	0	1	0	0	0
	S2	0	0	1	G1+G3+G4	SERR	1	0	1	0	1	0	0	0
	S3	0	1	1	G1'G2'G3'G4'	S4	0	1	0	0	0	1	0	0
	S3	0	1	1	G1'G2'G3'G4'	SOK	1	0	0	0	0	1	0	0
	S3	0	1	1	G1+G2+G4	SERR	1	0	1	0	0	1	0	0
	S4	0	1	0	G1'G2'G3'G4'	S1	0	0	0	0	0	0	1	0
	S4	0	1	0	G1'G2'G3'G4'	SOK	1	0	0	0	0	0	1	0
	S4	0	1	0	G1+G2+G3	SERR	1	0	1	0	0	0	1	0
	SOK	1	0	0	G1+G2+G3+G4	SOK	1	0	0	0	0	0	0	0
	SOK	1	0	0	G1'G2'G3'G4'	S1	0	0	0	0	0	0	0	0
	SERR	1	0	1	G1+G2+G3+G4	SERR	1	0	1	0	0	0	0	1
	SERR	1	0	1	G1'G2'G3'G4'	S1	0	0	0	0	0	0	0	1

20 of 22

Transition Equations

- Obtained from the transition list—**transition equations**:

$$Q1^* = Q2' \cdot Q0 \cdot G1' \cdot G2' \cdot G3' \cdot G4'$$

$$Q0^* = Q2' \cdot Q1' \cdot Q0' \cdot (G1' \cdot G2' \cdot G3' \cdot G4')$$

$$+ Q2' \cdot Q1' \cdot Q0' \cdot (G2 + G3 + G4)$$

$$+ Q2' \cdot Q1' \cdot Q0 \cdot (G1' \cdot G2' \cdot G3' \cdot G4')$$

$$+ Q2' \cdot Q1' \cdot Q0 \cdot (G1 + G3 + G4)$$

$$+ Q2' \cdot Q1 \cdot Q0 \cdot (G1 + G2 + G4)$$

$$+ Q2' \cdot Q1 \cdot Q0' \cdot (G1 + G2 + G3)$$

$$+ Q2 \cdot Q1' \cdot Q0 \cdot (G1 + G2 + G3 + G4)$$

$$Q2^{*'} = (Q2' + Q1') \cdot (G1' \cdot G2' \cdot G3' \cdot G4') \quad \leftarrow \text{formulated for "0"s}$$

- Moore machine → outputs independent of transition expressions → only one row of transition list must be considered for each current state

- Output equations:**

$$L1 = Q2' \cdot Q1' \cdot Q0' \quad L3 = Q2' \cdot Q1 \cdot Q0 \quad ERR = Q2 \cdot Q1' \cdot Q0$$

$$L2 = Q2' \cdot Q1' \cdot Q0 \quad L4 = Q2' \cdot Q1 \cdot Q0'$$

21 of 22

Unused States

- Guessing machine state diagram has 6 states, but 3 flip-flops have 8 states
- Omitted unused states implicitly treated as “don’t-cares” in next state equations:
 - Equations for $Q1^*$ and $Q0^*$ written as sum of transition p-terms for state/input combinations with explicit “1” in $Q1^*$ and $Q0^*$ columns
 - Unused states implicitly assumed to have “0” in $Q1^*$ and $Q0^*$ columns
 - Equation for $Q2^{*'}$ written as a sum of transition p-terms for state/input combinations with explicit “0” in $Q2^*$ column
- As a consequence, all unused states have a coded next state of “100” for all input combinations
== coding for **SOK** state
- This is safe & acceptable, but could treat them explicitly as “don’t-cares” – see Wakerly, 4th ed., page 583

22 of 22