

# 14:332:231 DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University  
Electrical & Computer Engineering  
Fall 2013


Lecture #22: Introduction to Verilog

## Hardware Description Languages

- Basic idea:
  - Language constructs describe circuits with two basic forms:
  - Structural descriptions:** connections of components (gates & flip-flops). Nearly one-to-one correspondence with schematic diagram (*circuit structure*).
  - Behavioral descriptions:** use statements (assignments and tests of logical conditions) to describe the relationships between inputs and outputs (*circuit function*).
- Originally invented for simulation
  - Now “logic synthesis” tools exist to automatically convert from HDL source to circuits.
  - High-level constructs greatly improve designer productivity.
  - However, this may lead to a false belief that hardware design is the same as writing programs!\*

“Structural” example:
 
```
Decoder(output x0,x1,x2,x3; inputs a,b)
{
    wire a_L, b_L;
    inv(b_L, b);
    inv(a_L, a);
    and(x0, a_L, b_L);
    and(x1, a_L, b);
    and(x2, a, b_L);
    and(x3, a, b);
}
```




“Behavioral” example:

```
Decoder(output x0,x1,x2,x3; inputs a,b)
{
    case [a b]
        00: [x0 x1 x2 x3] = 0x1;
        01: [x0 x1 x2 x3] = 0x2;
        10: [x0 x1 x2 x3] = 0x4;
        11: [x0 x1 x2 x3] = 0x8;
    endcase;
}
```

\* Describing hardware with a language is similar, however, to writing a parallel program.


# Sample Design Methodology

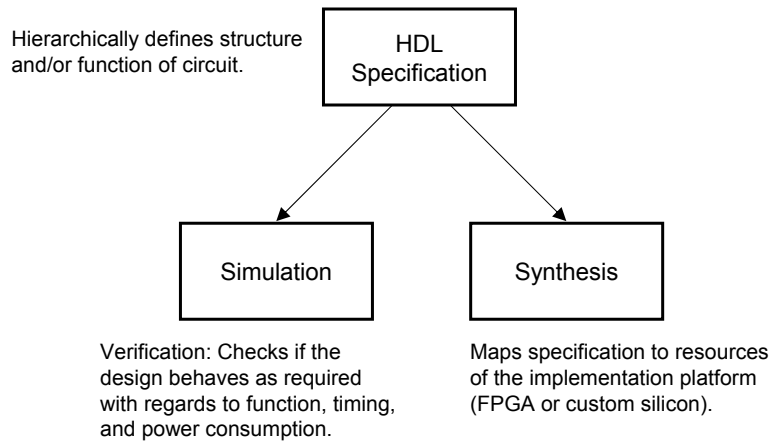

3 of 21
 
# Top-Down Architecture (1)


- Top Down Refinement Process
- Start Here:



4 of 21

## Top-Down Architecture (2)

- End Here:

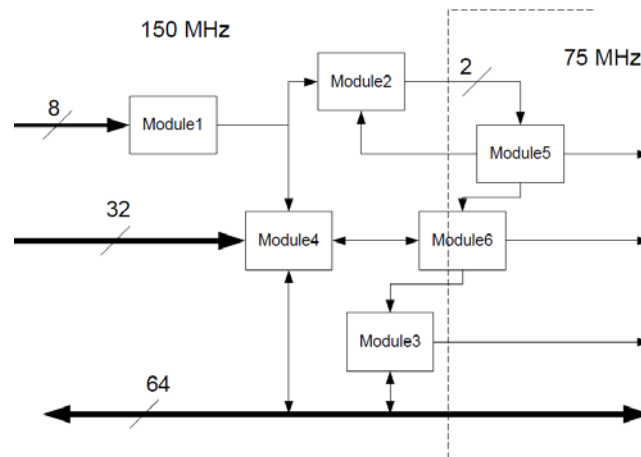

5 of 21

## History of the Verilog HDL

- **1984:** Gateway Design Automation introduced Verilog-XL
  - digital logic simulator
  - The Verilog language was part of the Verilog-XL simulator
  - The language was mostly created by 1 person, Phil Moorby
  - The language was intended to be used with only 1 product
- **1989:** Gateway merged into Cadence Design Systems
- **1990:** Cadence made the Verilog HDL public domain
- **1995:** The IEEE standardized the Verilog HDL (IEEE 1364)
- **2001:** The IEEE enhanced the Verilog HDL for modeling scalable designs, deep sub-micron accuracy, etc.
- **2005:** The IEEE added minor corrections, spec clarifications, and a few new language features
- **2009:** The IEEE standardized SystemVerilog, with many new features and capabilities to aid design verification and design modeling

6 of 21


# Verilog Introduction

- A module definition describes a component in a circuit
- Two ways to describe module contents:
  - Structural Verilog
    - Lists sub-components and how they are connected
    - Just like schematics, but using text
    - Tedious to write, hard to understand
    - You get precise control over circuit details
    - May be necessary to map to special resources of the FPGA
  - Behavioral Verilog
    - Describes what a component does, not how it does it
    - Synthesized into a circuit that has this behavior
    - Result is only as good as the tools
- Build up a hierarchy of modules. Top-level module is your entire design (or the test environment for your design).


7 of 21
 
# Verilog Modules

- Verilog modules are the building blocks for Verilog designs



- One module

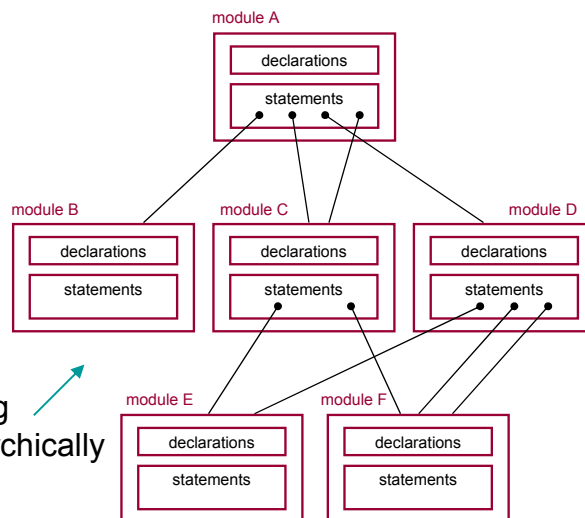


- Modules instantiating other modules hierarchically

8 of 21
 
# Contents of a Verilog Module


- Modules may represent:
  - An entire design
  - Major hierarchical blocks within a design
  - Individual components within a design
- Modules are completely self contained
  - The only things “global” in Verilog are the names of modules and primitives
  - Verilog does not have global variables or functions



9 of 21
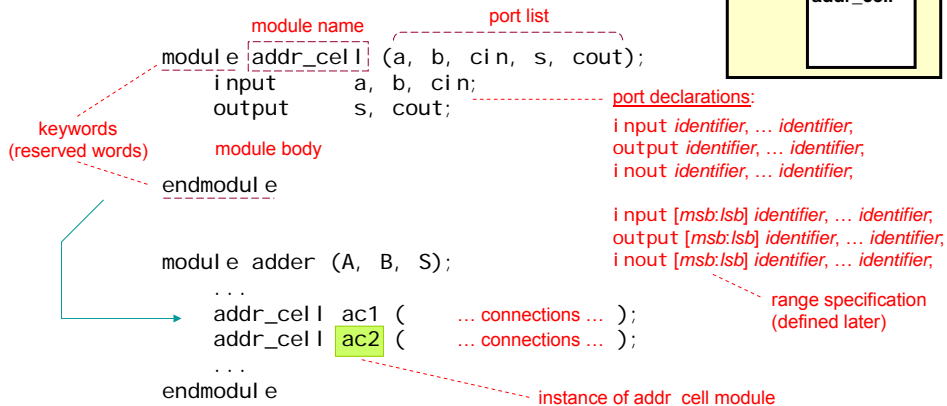
# Verilog Modules and Instantiation

- Modules define circuit components
- Instantiation defines hierarchy of the design



Note: A module is not a function in the C sense. There is no call and return mechanism. Think of it more like a hierarchical data structure.

10 of 21

## Verilog Modules and Instantiation

- Verilog supports ANSI C style port declarations
  - The port direction and data type of the signal can be included in the port list

```
                                port list
module addr_cell (input wire a,
                  input wire b,
                  input wire cin,
                  output reg sum, cout);
                                module body
endmodule

module adder (A, B, S);
...
addr_cell ac1 (... connections ...);
addr_cell ac2 (... connections ...);
...
endmodule                                instance of addr_cell module
```

11 of 21

## Verilog Logical System

- Verilog uses four-valued logic system
- A 1-bit signal can take on one of 4 values:
  - 0 Logical 0, or false
  - 1 Logical 1, or true
  - x An unknown/undefined logical value
  - z High impedance (floating), as in three-state logic
- Verilog has built-in *bitwise boolean operators* (see table in a later slide)

12 of 21

# Verilog Nets and Wires

- Verilog has two classes of signals: *Nets* and *Variables*
- A **net** corresponds to a wire in a physical circuit and provides connectivity between modules
  - **wire** is the default Net type
    - 'wire' is any signal name that appears in a module's input/output port list, but not in module's net declaration
    - 'wire' can be a *scalar* (single connection) or a *vector* (multiple connection)
- Verilog **net** types: **wire**, **tri**, **triand**, **trior**, **tri0**, **tri1**, **triereg**, **wand**, **wor**, **supply0**, **supply1**
  - supply0, supply1 are considered to be permanently wired to the power rail
  - 'wire' is conventionally used when a single driver is present
  - 'tri' is used when multiple drivers are present
    - When a 'tri' net is driven to a single value by  $\geq 1$  drivers, it takes on that value
    - When a 'tri' net is undriven, it floats (value 'z')
    - When it's driven to different values (0, 1, or x) by different drivers, it is in contention (value 'x')
- 'wire' is obsolete in SystemVerilog; instead, use the **logic** signal type

13 of 21

# Verilog Internal Variables


- Internal variables store values during a Verilog module's execution
  - They are neither inputs nor outputs, but are used only internal to the module
  - Don't have physical significance in a circuit
  - Used when describing circuit's behavior, in "procedural code" when we need to break a complex function into intermediate steps
- A variable can be assigned value in one Verilog statement; retains this value until overwritten in a later statement
  - Unlike a Net, a variable's value can be changed only within procedural code in a module, not from outside the module
  - **Input & inout ports** of a module cannot be variables; they must be 'net' types (e.g., 'wire')
  - **Output ports** can be either be 'net' or variable ('reg') types
- Two common types of variables:
  - **reg** (in old Verilog, but **logic** in SystemVerilog)
  - **integer** (used as loop control variables, e.g., in **for** loops)
- 'reg' is **NOT** a register or flip-flop
  - It's just a variable used on the left hand side of  $\leq$  or  $=$  assignment statements
  - It's replaced with **logic** in SystemVerilog

14 of 21

# Verilog Numbers
 
## Constants / Literals

- 14 ordinary decimal number
- 14 2's complement representation
- 12' b0000\_0100\_0110 12-bit binary number ("\_" is ignored)
- 12' h046 12-bit hexadecimal number
- 4' bx 4-bit binary number with unknown value xxxx
- 8' hfx 8-bit hexadecimal number, equivalent to 8' b1111\_xxxx



## Parameter declaration for defining named constants

```
parameter BUS_SIZE = 32, MSB = BUS_SIZE-1;
```

## Signal values

- By default, Values are unsigned
  - e.g., `C[4:0] = A[3:0] + B[3:0];`
  - if A = 0110 (6) and B = 1010(-6) then C = 10000 not 00000
  - i.e., B is zero-padded, not sign-extended

```
wire signed [31:0] x;
```

Declares a signed (2's complement) signal array.

15 of 21

# Vectors and Bit Selection

- Vector** is a group of individual 1-bit signals
  - Nets, variables, and constants can all be vectors
  - Examples:

```
reg [7:0] byte1, byte2, byte3;  
reg [15:0] word1, word2;  
reg [1:16] Zbus;
```
  - Note: in SystemVerilog use `logic` instead of `reg`
- Bit select** syntax to select individual bits
  - Example: `byte1[7]` selects the leftmost bit
- Part select** selects a range of bits
  - Example: `byte1[5:2]` selects the middle 4 bits

16 of 21



# Verilog Operators (1)

- **Concatenation operator { }** joins together two or more bits or vectors into a single vector
  - Example: {2' b00, 2' b11} produces {4' b0011}
- **Replication operator n{ }** replicates a bit or vector *n* times
  - Example: {2{byte1}, 2{byte2}} produces a 32-bit vector {byte1, byte1, byte2, byte2}
  - “Bit swizzling”: using bit/part select and concatenation to form busses
    - Example: {c[2:1], {3{d[0]}}, c[0], 3' b101} forms a 9-bit bus  $c_2c_1d_0d_0d_0c_0101$
- See next-slide table for more operators
- **Padding:** vectors of different sizes are aligned on their rightmost bits and padded with zeros at left
  - Example: 2' b11 & 4' b0101 produces 4' b0001

17 of 21

# Verilog Operators (2)

Verilog Operator	Name	Functional Group
[ ]	bit-select or part-select	
( )	parenthesis	
!	logical negation	Logical
-	negation	Bit-wise
&	reduction AND	Reduction
	reduction OR	Reduction
~&	reduction NAND	Reduction
~	reduction NOR	Reduction
^	reduction XOR	Reduction
~^ or ~^	reduction XNOR	Reduction
+	unary plus (sign)	Arithmetic
-	unary minus (sign)	Arithmetic
{ }	concatenation	Concatenation
{ { } }	replication	Replication
*	multiply	Arithmetic
/	divide	Arithmetic
%	modulus	Arithmetic
+	binary plus (addition)	Arithmetic
-	binary minus (subtraction)	Arithmetic
<<	shift left	Shift
>>	shift right	Shift

<<<	arithmetic shift left	Arithmetic
>>>	arithmetic shift right	Arithmetic
>	greater than	Relational
>=	greater than or equal to	Relational
<	less than	Relational
<=	less than or equal to	Relational
==	logical equality	Equality
!=	logical inequality	Equality
===	case equality	Equality
!==	case inequality	Equality
&	bit-wise AND	Bit-wise
^	bit-wise XOR	Bit-wise
~^ or ~^	bit-wise XNOR	Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional

18 of 21

## Verilog Operators (3)

- Built-in **arithmetic operators** treat vectors as unsigned integers;  
leftmost bit of a vector is MSB
- **Shift operator** shifts the 1<sup>st</sup> operand by a number of positions given by the 2<sup>nd</sup> operand
  - Example: `8' b11010011<<3` gives `8' b10011000`
- **Boolean reduction operators** take a single vector operand and collapse it to a 1-bit result
  - Reduction operators combine all bits in the vector and return a 1-bit result
  - Example: `^word` produces `1' b1` if odd number of bits of 'word' are 1 (*parity calculation* using XOR operation `^`)

19 of 21

## Verilog Operators (4)

### Arithmetic Shift Operators

- The `>>>` token does an **arithmetic shift right**, filling with the value of the **sign bit**
  - Different than the `>>` bit shift right operator, which always fills with **zero**
- The `<<<` token does an **arithmetic shift left**, filling with zeros
  - Same functionality as the `<<` bit shift left operator

### Example:

– Given: `in = 8' b11001010;`

```
assign out = in >> 3;  
//bit shift right results in 8' b00011001
```

```
assign out = in >>> 3;  
//arithmetic shift right results in 8' b11111001
```

20 of 21

## Verilog Operators (5)

"case equality" operator `===`

- `==` tests **logical equality**  
(tests for 1 and 0, all other will result in x)
- `===` tests 4-state logical equality  
(tests for 1, 0, z and x)
- Example, after executing `dataoutput = 52'bx`:
  - `if (dataoutput[7:0] == 8'bx) begin ...`
  - versus
  - `if (dataoutput[7:0] === 8'bx) begin ...`
- the second gives 1, but the first gives 0.
  - The result of `dataoutput == 8'bx` is not really "0", it is "x". However, both "0" and "x" are false values, meaning the body of the `if` will not be executed.
  - For the `===` and `!==` operators, bits with x and z are included in the comparison and must match for the result to be true.
  - So, `a == b` is 'a equals b' and `a === b` is 'a *really* equals b'

21 of 21