

# 14:332:231 DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University  
Electrical & Computer Engineering  
Fall 2013

Lecture #23: Verilog Structural and Behavioral Design


## Hardware Description Languages

[ Recall from Lecture #22 ]

- **Basic idea:**
  - Language constructs describe circuits with two basic forms:
  - **Structural descriptions:** connections of components (gates & flip-flops). Nearly one-to-one correspondence with schematic diagram (*circuit structure*).
  - **Behavioral descriptions:** use statements (assignments and tests of logical conditions) to describe the relationships between inputs and outputs (*circuit function*).

“Structural” example:
 
```
Decoder(output x0,x1,x2,x3; inputs a,b)
{
    wire a_L, b_L;
    inv(b_L, b);
    inv(a_L, a);
    and(x0, a_L, b_L);
    and(x1, a_L, b);
    and(x2, a, b_L);
    and(x3, a, b);
}
```



“Behavioral” example:

```
Decoder(output x0,x1,x2,x3; inputs a,b)
{
    case [a b]
        00: [x0 x1 x2 x3] = 0x1;
        01: [x0 x1 x2 x3] = 0x2;
        10: [x0 x1 x2 x3] = 0x4;
        11: [x0 x1 x2 x3] = 0x8;
    endcase;
}
```

2 of 29

## Verilog Concurrent Statements

- Concurrent statements specify digital logic operation, from which a realization is synthesized; 3 common types:
  1. Instance statement
    - Instantiates a module, used in *structural* descriptions
    - Similar to a constructor call in OO languages (C++, Java, ...)
  2. Continuous assignment statement
    - For *behavioral* descriptions of *combinational* circuits
  3. always blocks (non-continuous assignments)
    - For *behavioral* descriptions of synchronous *sequential* circuits
- Concurrent statements “execute” *simultaneously* and *continuously*
  - Modeling the continuous operation of hardware where connected elements affect each other continuously, not just at particular, ordered time steps

3 of 29

## Verilog Built-in Gates

[ structural style ]

- Built-in gate names are reserved words
  - and, nand, or, nor** ~ any number of inputs per gate
  - xor, xnor**
  - buf** = 1-input noninverting buffer
  - not** = inverter
  - bufif0, bufif1** = 1-input buffer w/ tri-state out
  - notif0, notif1** = inverter w/ tri-state outputs
- Other predefined components include
  - AND-OR-INVERT (sum-of-products) gates
  - flip-flops, decoders, multiplexers, ...

4 of 29

# Verilog Instance Statement

[ structural style ]

- Two formats of instance statement:
  - `component-name instance-identifier ( expr, expr, ..., expr );` 1. defined port order
  - `component-name instance-identifier ( .port-name(expr),  
.port-name(expr),  
...,  
.port-name(expr) );` 2. named ports
- Multiple instances of the same component/module distinguished by unique names (“instance-identifier”)
- The 1<sup>st</sup> format depends on the order in which port names appear in the original component/module definition
  - Expressions listed in the same order as ports to which they connect
  - For built-in gates, the defined port order is (output, input, input, ...)
  - The order among the multiple inputs doesn't matter
  - For built-in three-state buffers and inverters, the defined order is (output, data-input, enable-input)
- The 2<sup>nd</sup> format explicitly names the ports
  - Recommended because it helps avoid mistakes in coding

5 of 29

# Structural Model - XOR example

[ structural style ]

```

module xor_gate ( out, a, b );
  input a, b;
  output out;
  wire a_L, b_L, t1, t2;

```


**instance statements:**

```

  not invA (a_L, a);
  not invB (b_L, b);
  and and1 (t1, a, b_L);
  and and2 (t2, b, a_L);
  or or1 (out, t1, t2);

```

built-in gates

 

endmodule

interconnections (note that output is first)



instance name/identifier (each must be unique w/in the module)

- Notes:
  - The instantiated gates are not “executed”. They are *always active*.
  - XOR gate already exists as a built-in (only an example – no need to define it)
  - Undeclared variables are assumed to be wires. Don't let this happen to you!

6 of 29

# Structural Example: 2-to-1 Mux

[ structural style ]

  

```

/* 2-input multiplexor in gates */
module mux2 (in0, in1, select, out);
  input in0, in1, select;
  output out;
  wire s0, w0, w1;
  not (s0, select);
  and (w0, s0, in0),
      (w1, select, in1);
  or (out, w0, w1);
endmodule // mux2

```

C/C++ style comments

built-ins don't need instance names

multiple instances can share the same "master" name



built-in gates can have > 2 inputs

Example:  
and (w0, a, b, c, d);

7 of 29

# Instantiation, Signal Array, Named Ports

[ structural style ]

  

```

/* 2-input multiplexor in gates */
module mux2 (in0, in1, select, out);
  input in0, in1, select;
  output out;
  wire s0, w0, w1;
  not (s0, select);
  and (w0, s0, in0),
      (w1, select, in1);
  or (out, w0, w1);
endmodule // mux2

```

```

module mux4 (in0, in1, in2, in3, selct, out);
  input in0, in1, in2, in3;
  input [1:0] selct;
  output out;
  wire w0, w1;
  mux2
    m_lo (. select(selct[0]), . in0(in0), . in1(in1), . out(w0)),
    m_hi (. select(selct[0]), . in0(in2), . in1(in3), . out(w1)),
    m_fin (. select(selct[1]), . in0(w0), . in1(w1), . out(out));
endmodule // mux4

```

Signal array. Declares selct[1], selct[0]

Named ports. Highly recommended.

multiple instances of same module

8 of 29

# Parameterized Module

[ structural style ]

- Parameterize structural modules to handle inputs and outputs of any width
  - Example: 3-input majority function
    - Outputs “1” if at least two inputs are “1”  
 $OUT = I0 \cdot I1 + I1 \cdot I2 + I2 \cdot I0$

```
module Maj (OUT, I0, I1, I2);  
  parameter WID = 1;  
  input [WID-1:0] I0, I1, I2;  
  output [WID-1:0] OUT;  
  
  assign OUT = I0 & I1 | I1 & I2 | I2 & I0;  
endmodule;
```
- When Maj module instantiated using regular syntax, the parameter WID takes on default value 1
- Instance statement allows parameter substitution using #
  - Example: X, Y, Z are 8-bit input vectors, the 8-bit majority function:  
`Maj #(8) U1 ( .OUT(W), .I0(X), .I1(Y), .I2(Z) );`

9 of 29

# Simple Behavioral Model

[ behavioral style ]

```
module and_gate (out, in1, in2);  
  input in1, in2;  
  output out;  
  
  assign out = in1 & in2;  
  
endmodule
```

& = AND  
| = OR  
^ = XOR

“continuous assignment”

connects out to be the AND of in1 and in2

- Shorthand for explicit instantiation of AND gate (in this case).
- The assignment happens *continuously* (modeling the continuous operation of hardware); therefore, any change on the right-hand-side (RHS) signals is reflected immediately on the output port (except for the small delay associated with the implementation of the “&” operation).
- Different from assignment in C that takes place when the program counter reaches that place in the program.

10 of 29

# Example: Ripple Adder

[ Recall from Lecture #14 ]


[ behavioral style ]

```

module FullAdder(a, b, ci, r, co);
  input a, b, ci;
  output r, co;

  assign r = a ^ b ^ ci;
  assign co = a&ci | a&b | b&cin;
endmodule
    
```

[ behavioral ]

 


Inputs			Outputs	
a	b	ci	r	co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

```

module Adder(A, B, R);
  input [3:0] A;
  input [3:0] B;
  output [4:0] R;

  wire c1, c2, c3;
  FullAdder
    add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),
    add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),
    add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),
    add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );
endmodule
    
```

[ structural ]

 

11 of 29

## Continuous Assignment Statements

[ behavioral style ]

- **assign** net-name = expression;
- **assign** net-name[bit-indx] = expression;
- **assign** net-name[msb:lsb] = expression;
- **assign** net-concatenation = expression;
  
- Continuous-assignment statements are evaluated *continuously* (because hardware elements affect each other continuously, not just at particular, ordered time steps)
- The *order* of continuous assignment statements in a module doesn't matter
- Continuous-assignment statement is unconditional, but different values can be assigned using the *conditional operator* ( ? : )

12 of 29

# Continuous Assignment Examples

[ behavioral style ]

```
wire [3:0] A, X, Y, R, Z;
wire [7:0] P;
wire r, a, cout, cin;
```

- assign R = X | (Y & ~Z); ← use of bit-wise Boolean operators
- assign r = &X; ← example reduction operator
- assign R = (a == 1'b0) ? X : Y; ← conditional assignment (= multiplexor)
- assign P = 8'hff; ← example constants
- assign P = X \* Y; ← arithmetic operators (use with care!)
- assign P[7:0] = {4{X[3]}, X[3:0]}; ← example: sign-extension
- assign {cout, R} = X + Y + cin; ← bit field concatenation
- assign Y = A << 2; ← bit shift operator
- assign Y = {A[1], A[0], 1'b0, 1'b0}; ← equivalent bit shift

13 of 29

# Non-continuous Assignments

[ behavioral style ]

## always blocks and procedural code

- Syntax of Verilog always blocks
  - always @(signal-name or ... or signal-name) procedural-statement

optional sensitivity list

- always procedural-statement

```
begin
    procedural-statement
    ...
    procedural-statement
end
```

- Procedural statements in an always block execute *sequentially*, as in software program
  - However, always blocks execute *concurrently* with other concurrent statements in the module
- Note: assign statements must be used outside always statements; both are evaluated concurrently

14 of 29

# Procedural Sensitivity Lists

[ behavioral style ]

- The execution of a statements within a procedure can be controlled using an event-control **sensitivity list**
  - An **always** procedure must re-evaluate the outputs whenever an “input” changes value
    - An “input” is any signal used to determine the value of assignments
- Procedures automatically become active at time zero
- Execution of statements is delayed until a change occurs on a signal in the “*sensitivity list*”

**always** @ ( <edge> <signal> or <edge> <signal> )

- <edge> may be **posedge** (positive) or **negedge** (negative)
  - If no **edge** is specified, then any transition is used
- Sensitivity to multiple signals is specified using an “or” separated list

15 of 29

# always Block Example (1)

[ behavioral style ]

- Sensitivity list signals @(. . . ) determine when the **always** block executes
  - The block is initially *suspended* and starts *executing* when any signal in the sensitivity list changes its value
  - This continues until the block executes without any sensitivity-list signal changing its value

```
module and_or_gate (out, in1, in2, in3);
  input in1, in2, in3;
  output out;
  reg out;
  always @ (in1 or in3)
  begin
    out = (in1 & in2) | in3;
  end
endmodule
```

keyword

“sensitivity” list, controls when the following statement is executed. Note that change in *in2* will NOT trigger the statement!

“begin-end block” brackets multiple procedural statements (not necessary in this example)


16 of 29


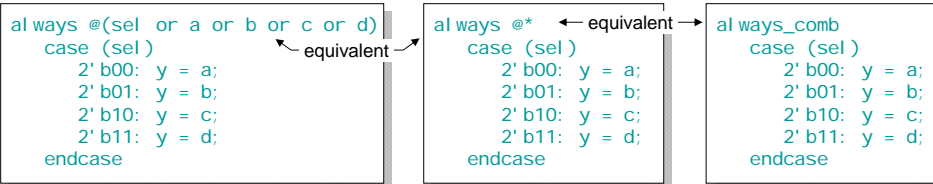
# A Combinational Logic Sensitivity

[ behavioral style ]

- Verilog features a “wildcard” token to indicate a *combinational logic sensitivity list*
  - The `@*` token is a time control which indicates that the control is automatically sensitive to any change on any “input” to the statement or group-of-statements that follows
    - An “input” is any signal whose value is read by the statement or statement group
- SystemVerilog introduced `always_comb` for modeling combinational logic
  - The simulator infers the sensitivity list to be all variables from the contained statements



Note: case statement is defined later.

17 of 29

# Verilog Procedural Statements

[ behavioral style ]

- **Blocking assignment:** `variable-name = expression;`
  - Evaluates the expression immediately and assigns to variable
- **Nonblocking assignment:** `variable-name <= expression;`
  - Evaluates the expression immediately but does NOT assign to variable until an infinitesimal delay after the `always` block has completed execution
- **begin-end block**
  - Encloses a list of procedural statements that execute *sequentially*
- **if statement**
  - A *condition* (logical expression) is tested; if true the enclosed statement is executed
- **case statement**
  - A “selection expression” followed by a list of “choices” and corresponding procedural statements
- **Looping statements:** `for`, `while`, `repeat`
  - Execute the enclosed procedural statements for a given number of iterations

18 of 29

# Blocking vs. Nonblocking Statements

[ behavioral style ]

## ■ Blocking assignment:

`variable-name = expression;`

- “immediate assignment” or within a specifiable delay
- Evaluates the expression immediately and assigns to variable
- Use **blocking** assignments to create **combinational** logic

## ■ Nonblocking assignment:

`variable-name <= expression;`

- “nonblocking and slightly deferred assignment” or “late assignment”
- Evaluates the expression immediately but does NOT assign to variable until an infinitesimal delay after the `always` block has completed execution
- Use **nonblocking** assignments to create **sequential** logic

19 of 29

# always Block Example (2)

[ behavioral style ]

- Sensitivity list signals `@(...)` determine when the `always` block executes
  - For example, the flip-flop includes only `clk` in the sensitivity list
  - Flip-flop remembers its old value of `q` until the next rising edge of the `clk`, even if `d` changes in the interim
  - In contrast, continuous assignment statements (`assign`) are reevaluated anytime any of the inputs on the right hand side changes therefore, such code necessarily describes combinational logic

```
module register ( //a vector of flip-flops
    input logic clk,
    input logic [3:0] d;
    output logic [3:0] q );
    always_ff @(posedge clk)
        q <= d;
endmodule
```

keyword in SystemVerilog

“sensitivity” list, triggers the action in the statement body

nonblocking assignment

- SystemVerilog introduced `always_ff`, `always_latch`, and `always_comb` (seen above) to imply flip-flops, latches, or combinational logic
- This reduces the risk of common errors

20 of 29

# if statement

[ behavioral style ]

- A *condition* (logical expression) is tested; if true the enclosed procedural statement is executed
- **Nested** if-else example:

```
module mux4 (in0, in1, in2, in3, select, out);
  input in0, in1, in2, in3;
  input [1:0] select;
  output out;
  reg out;

  always @(in0 in1 in2 in3 select)
    if (select == 2'b00) out=in0;
      else if (select == 2'b01) out=in1;
        else if (select == 2'b10) out=in2;
          else out=in3;
endmodule // mux4
```

- Nested if structure leads to “priority logic” structure, with different delays for different inputs (*i n3* to *out* delay > than *i n0* to *out* delay). *case* statement treats all inputs the same ...

21 of 29

# case statement

[ behavioral style ]

- Evaluates the “selection expression,” finds the first “choice” that matches the expression’s value and executes the corresponding procedural statement
- *case* statement example:

```
module mux4 (in0, in1, in2, in3, select, out);
  input in0, in1, in2, in3;
  input [1:0] select;
  output out;
  reg out;

  always @(in0 in1 in2 in3 select)
    case (select)
      2'b00: out=in0;
      2'b01: out=in1;
      2'b10: out=in2;
      2'b11: out=in3;
    endcase
endmodule // mux4
```

Recall that we could use a “wildcard” token \* to indicate a combinational logic sensitivity list or *always\_comb* in SystemVerilog

```
always @*
  case (select)
    ...
  endcase
```

The statement(s) corresponding to whichever constant matches “select” get applied.

22 of 29

# Incomplete case statement

[ behavioral style ]

- Listed choices may not be “all inclusive”—some possible values of the selection expression may be missing
- Incomplete case statement example:

```
module mux3 (in0, in1, in2, select, out);
  input in0, in1, in2;
  input [1:0] select;
  output reg out;

  always @ (in0 in1 in2 select)
    case (select)
      2' b00: out=in0;
      2' b01: out=in1;
      2' b10: out=in2;
    endcase
endmodule // mux3
```

If sel = 2' b11 = 3, mux will output the previous value!  
—inferred an unwanted latch

Inferring an unwanted latch can be prevented with a default statement:  
default: out=1' bx;

23 of 29

# for loop statement

[ behavioral style ]

- Syntax of a Verilog for statement:  
*for ( loop-index = first-expr, logical expression; loop-idx = next-expr )  
procedural-statement*
- for statement example — prime-number detector:

```
module Vprimebv (input [15:0] N, output reg F);
  reg prime;
  integer i;

  always @ (N) begin
    prime = 1; // initial value
    if ( (N==1) || (N==2) ) prime = 1; // special cases
    else if ( (N % 2) == 0 ) prime = 0; // even, not prime
    else for ( i = 3; i <= 255; i = i+2 ) // i = loop-index
      if ( (N % i) == 0 ) && (N != i)
        prime = 0; // set to 0 if N is divisible by any i
    if (prime==1) F = 1; else F = 0;
  end
endmodule // Vprimebv
```

keyword

for statement

24 of 29


## Behavioral vs. Structural

- Rule of thumb:
  - Behavioral doesn't have sub-components
  - Structural has sub-components:
    - Instantiated Modules
    - Instantiated Gates
    - Instantiated Primitives
- Most levels are mixed

25 of 29

## Behavioral Example


- Behavioral only
- No instantiations

 

26 of 29

 
# Behavioral and Structural

- Behavioral:
  - Adder function
  - Register function
- Structural:
  - Top module
  - Two instantiations



27 of 29

# Structural Low-level Details

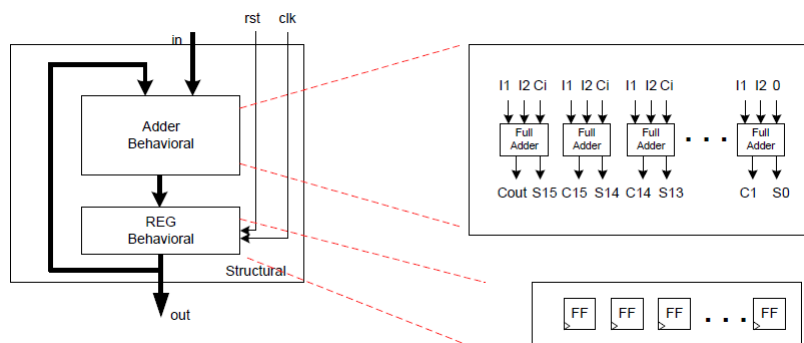

28 of 29

## Design Strategy

- Generally, complex systems are designed *hierarchically*
- The overall system is described *structurally* by instantiating its major components (“subsystems”)
- Each subsystem is described structurally from its building blocks ...
- Continued recursively until pieces are simple enough to describe *behaviorally*
- Recommended to avoid (at least minimize) mixing structural and behavioral descriptions within a single module

29 of 29