

14:332:231

DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University
Electrical & Computer Engineering
Fall 2013

Lecture #8: Timing Hazards

Gate Delays

- When the input to a logic gate is changed, the output will *not* change immediately.
- The switching elements within a gate take a finite time to react to a change (**transition**) in input.
- As a result the change in the gate output is delayed w.r.t. to the input change.
- Such delay is called the **propagation delay** of the logic gate (t_p)
- The propagation delay for a 0-to-1 output change (t_{pLH}) may be different than the delay for a 1-to-0 change (t_{pHL}).

2 of 21

[RECALL from Lecture #1] Transition Delays


(a) Ideal case of zero-time switching:



(b) A more realistic approximation:



 
(c) Actual timing for rise (t_r , low-to-high) and fall (t_f , high-to-low) times:




3 of 21

Propagation Delays for a CMOS Inverter

(a) Ignoring rise and fall times:

 

 (b) Measured at midpoints of transitions:



4 of 21


Effect of Gate Delays

- The analysis of a combinational circuit ignoring delays can predict only its **steady-state behavior**
 - Predicts a circuit's output as a function of its inputs assuming that the inputs have been stable for a long time, relative to the delays in the circuit's electronics.
- Because of circuit delays, the **transient behavior** of a combinational logic circuit may differ from what is predicted by steady-state analysis.
- **Timing hazard**: a circuit's output may produce a short pulse ("glitch") at a time when steady state analysis predicts that the output should not change.

5 of 21

Timing Hazard


- A gate has measurable response time t_{pLH} and t_{pHL} . Around 10ns per gate.
- Delays through transmission gates can add up and introduce timing hazards.
- t_{pLH} = low-to-high, t_{pHL} = high-to-low propagation times
- **static-1 hazard** is a short "0" *glitch* when for a changed input, we expect (by logic theorems) the output to remain constant "1".
- **static-0 hazard** is a short "1" *glitch* when we expect the output to remain constant "0".

 

6 of 21

Circuit with a Static-1 Hazard


Ideal scenario:

 

- Assume: $X, Y, Z = 111$
- Consider a transition to $X, Y, Z = 110$
- What we logically expect:


$$F = X \cdot Z' + Y \cdot Z$$

 - Before: $F = 1 \cdot (1)' + 1 \cdot 1 = 1 \cdot 0 + 1 = 1$
- After: $F = 1 \cdot (0)' + 1 \cdot 0 = 1 \cdot 1 + 0 = 1$
- \rightarrow **No change** in the output !!



7 of 21


Real World Gates Introduce Delays

 

- Input signal of each gate is shifted in the output by a constant delay

8 of 21

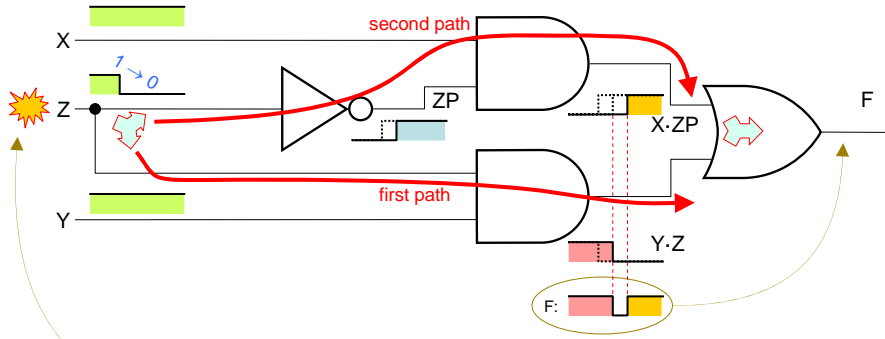Different Paths Introduce Different Delays




Change occurs at input Z and propagates to output F along two paths with different delays

Basically because of gate delays for a moment when input changes it is not true that $A + A' = 1$!


9 of 21

Circuit with a Static-1 Hazard

Real world:

 

Assume: $X=1$ $Y=1$ $Z=1 \rightarrow 0$

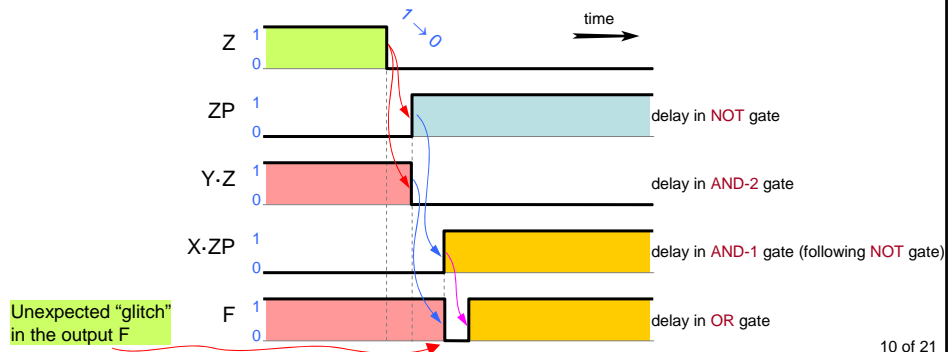

10 of 21

Timing Hazards and Karnaugh Maps

- Recall that in Sum-of-Products (AND-OR) circuits, AND gates correspond to prime implicants of the Karnaugh map
- A potential hazard exists wherever two adjacent 1-cells in a Karnaugh map are not covered by a single product term (prime implicant)
- A hazard occurs when there is a transition between adjacent prime implicants

11 of 21

Eliminating the Timing Hazard

- To eliminate hazards, find a cover in which all adjacent 1-cells are covered by a prime implicant
- Define “consensus” prime implicant, as a product term not covered in F
- Therefore, include an extra product term to cover the hazardous input combination

12 of 21

Eliminating the Timing Hazard

Minimal cost $F = X \cdot Z' + Y \cdot Z$
 (these adjacent 1-cells are NOT covered \rightarrow 1-hazard)

$F = X \cdot Z' + Y \cdot Z + X \cdot Y$
 (consensus term)

A "redundant" term was introduced.

13 of 21

So, How Does This Help?



- Unexpected "glitch" is eliminated !

A change in input variable Z causes a transition between two adjacent 1-cells but now these 1-cells are included in the product term X·Y

14 of 21


Why This Works

  Because the consensus term $X \cdot Y$ fills in (“covers”) the temporary gaps during switching from one active AND gate (e.g., $X \cdot Z'$) to another (e.g., $Y \cdot Z$)




15 of 21

Another Example (four variables)

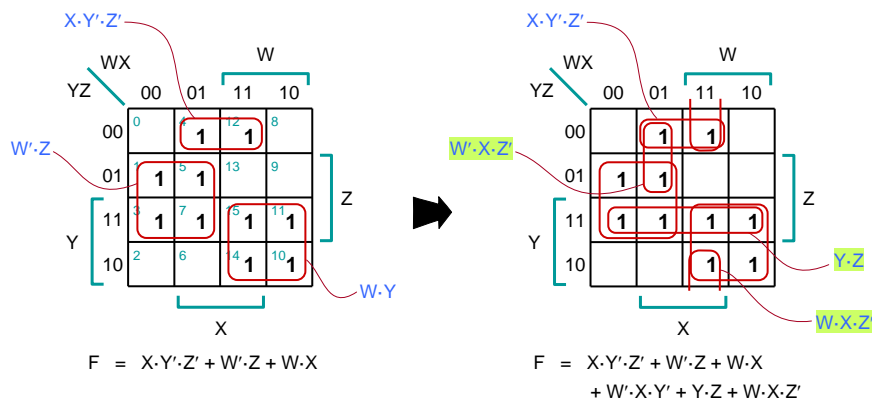

16 of 21


Circuit with a Static-0 Hazard

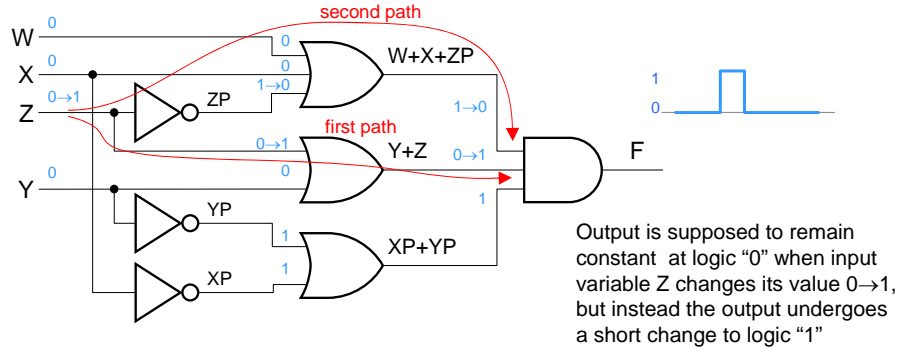

Product of sums: static-0 hazard

17 of 21

Circuit with a Static-0 Hazard

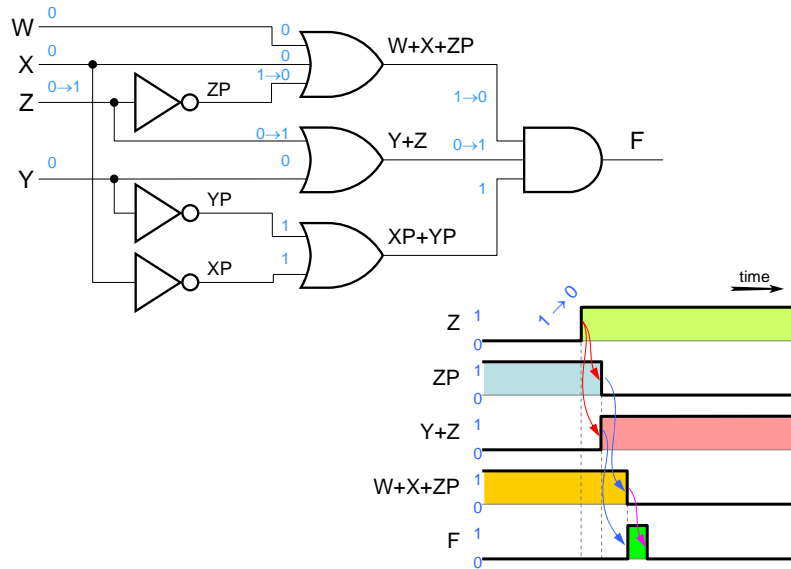


18 of 21

Dynamic Hazards

- **Dynamic hazard:** Output signal is supposed to change $1 \rightarrow 0$ or $0 \rightarrow 1$ but a short oscillation occurs before the output settles to its new logic value.
- Occurs if there are *multiple paths* with *different delays* from the changing input to the changing output.
- In practice many input variables, multiple outputs;
solved by computer programs

19 of 21


Example of Dynamic Hazard

 

Change occurs at input X and propagates to output F along **three paths** with different delays

20 of 21

Example of Dynamic Hazard

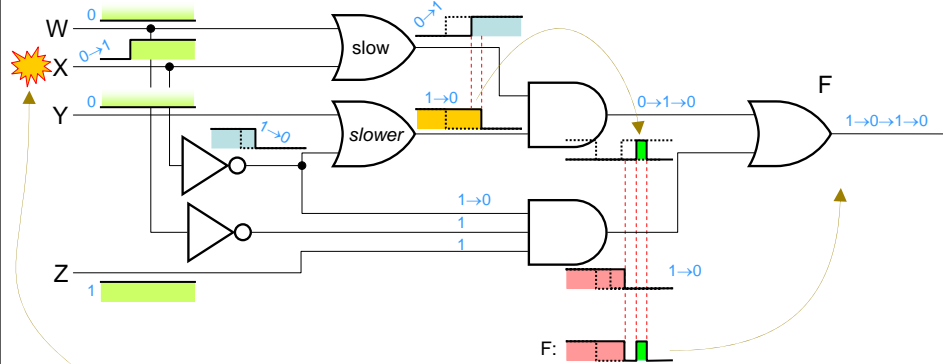

Change occurs at input X and propagates to output F along **three paths** with different delays