

# 14:332:231 DIGITAL LOGIC DESIGN

Ivan Marsic, Rutgers University  
Electrical & Computer Engineering  
Fall 2013

Lecture #9: Combinational Logic Design Practices

## Signal Names and Active Levels


- Signal names are chosen to be descriptive
- Active levels -- HIGH or LOW
  - Named condition or action occurs in either the HIGH or the LOW state, according to the active-level designation in the name.

<i>Active Low</i>	<i>Active High</i>
READY-	READY+
ERROR.L	ERROR.H
ADDR15(L)	ADDR15(H)
RESET*	RESET
ENABLE~	ENABLE
~GO	GO
/RECEIVE	RECEIVE
TRANSMIT_L	TRANSMIT


we will use this notation →

2 of 26


# Errors and Active Levels

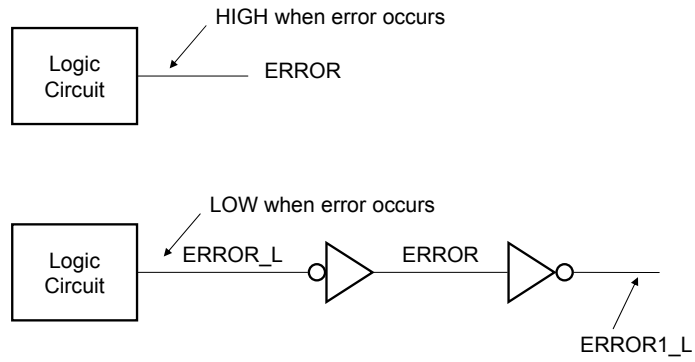

# Flat Schematic Structure

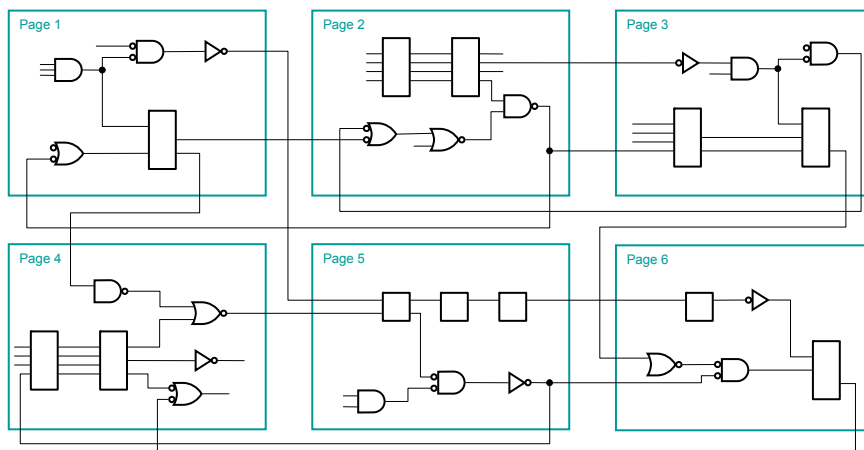


# Hierarchical Schematic Structure

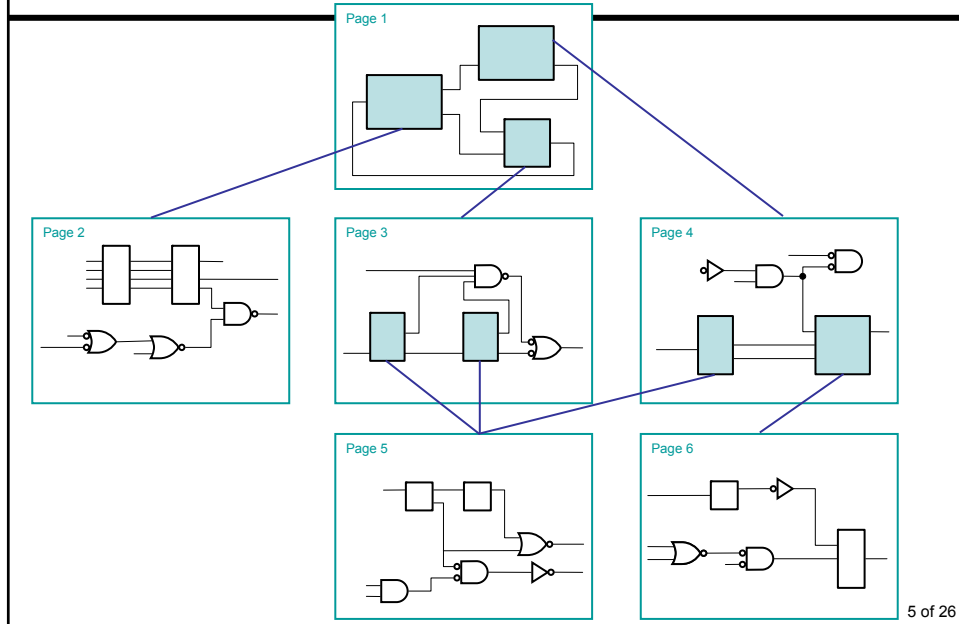

 
## Buffer

- A buffer is a gate with the function  $F = X$ :




- In terms of Boolean function, a buffer is the same as a wire connection!
- So why use it?
  - A buffer is an electronic **amplifier** used to improve circuit voltage levels and increase the speed of circuit operation.

## Gate Symbols [recall Lecture #4]

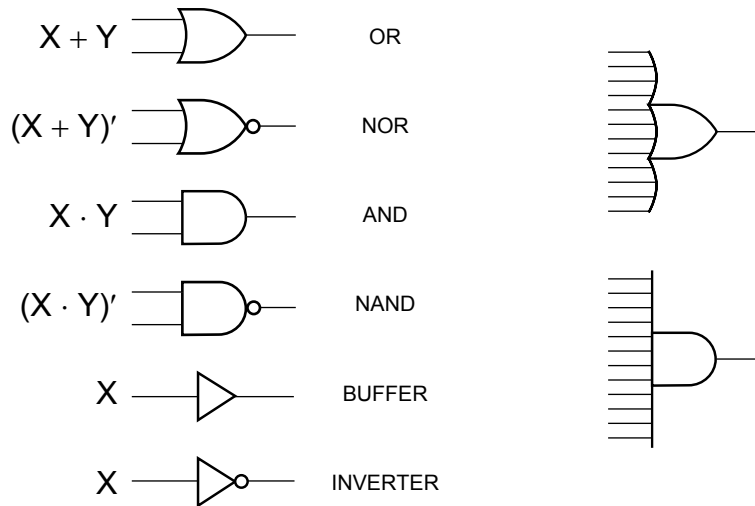

7 of 26

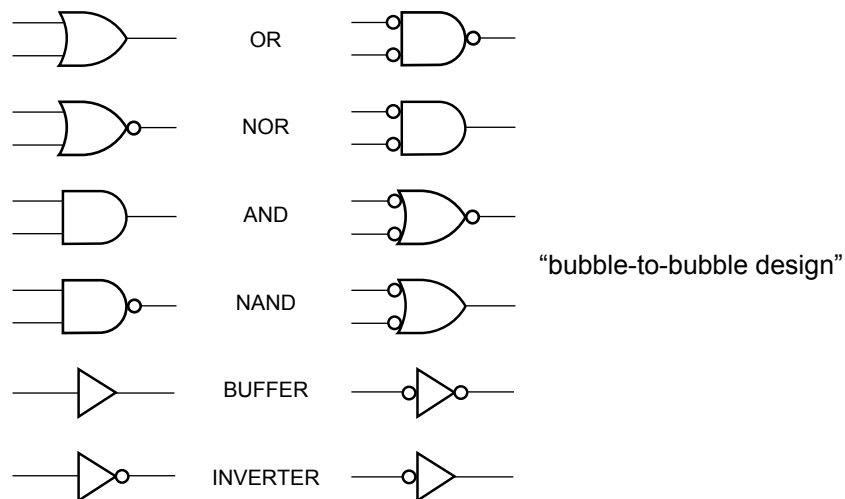
## DeMorgan Equivalent Symbols [Lecture #4]



- Which symbol to use?
- Answer depends on signal names and active levels

8 of 26


# Example Schematic

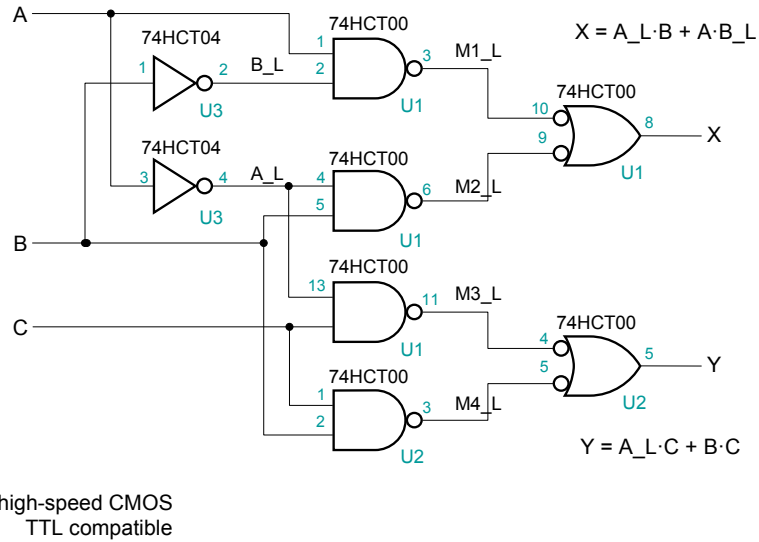

9 of 26


# Circuit Timing

Circuit block diagram:

 


ENB (enable) is constant

causality and propagation delay:

 

minimum and maximum delays:

 


another graph for the ENB input ...


10 of 26

## Timing Diagrams for "Data" Signals

Certain and uncertain transitions:

 

Sequences of values on an 8-bit bus:

 

11 of 26


## Gates w/ Special I/O Characteristics

- Schmitt-trigger inputs (Wakerly, Section 3.7.2, page 130)
  - A special circuit that uses feedback internally to shift the switching threshold depending on whether the input is changing LOW-to-HIGH or HIGH-to-LOW ("hysteresis")
- Three-state outputs (Wakerly, Section 3.7.3, page 132)
  - Output has a third electrical state (not logic state), called *high-impedance*, *Hi-Z*, or *floating state*
  - In this state, the output behaves as if it isn't even connected to the circuit—the device output "floats" as if it weren't even there
- Open-drain (open collector) outputs (Wakerly, Section 3.7.4, page 133)
  - The output usually comprises an external pull-up resistor, which raises the output voltage when the transistor is turned off
  - Can be rated to withstand a higher voltage than the chip supply voltage
  - Commonly used to drive devices such as Nixie tubes, vacuum fluorescent displays, relays or motors that require higher operating voltages than the usual 5-Volt logic supply

12 of 26

 
# Open-drain (open-collector) outputs

- *p*-channel transistor provides *active pull-up* of the output voltage on a LOW-to-HIGH transition
- Omitted in gates with *open-drain outputs* (see NAND gate below) [called “open-collector” in TTL]
- Example use: driving a light-emitting diode (LED)



Open-drain CMOS NAND gate

A	B	Q1	Q2	Z
L	L	off	off	open
L	H	off	on	open
H	L	on	off	open
H	H	on	on	L

 


Driving an LED with an open-drain output

13 of 26

 
# Schmitt-Trigger Inverter

It has a *hysteresis* (difference between the two thresholds) of 0.8 Volts between the low-to-high and high-to-low inputs.


a regular inverter input-output transfer characteristic:



 Schmitt-trigger input-output transfer characteristic:




Schmitt-trigger inverter logic symbol:

 


14 of 26

## Device Operation w/ Noisy Inputs

noisy, slowly-changing input:

 

ordinary inverter:

 

Schmitt-trigger inv.:  
(0.8 V hysteresis)




15 of 26


## Enabling Function

- **Enabling** permits an input signal to pass through a circuit to an output
- **Disabling** blocks an input signal from passing through to an output, replacing it with a fixed value
- The value on the output when it is disabled can be Hi-Z (as for three-state buffers and transmission gates, described next), "0", or "1"

– When disabled, "0" output

 

– When disabled, "1" output

 


16 of 26



# Three-State Buffers (a.k.a. Drivers)


- For the symbol and truth table, IN is the **data input**, and EN, the **control input**.
- For EN = 0, regardless of the value on IN (denoted by X), the output value is Hi-Z.
- For EN = 1, the output value follows the input value.
- Variations:
  - Data input, IN, can be inverted
  - Control input, EN, can be inverted by addition of "bubbles" to signals.

Symbol:

 


Truth table:

EN	IN	OUT
L	L	Hi-Z
L	H	Hi-Z
H	L	L
H	H	H

 

**OUT = IN · EN**  
 (logic function, but ignores non-logic connectivity control) 17 of 26

# Different Flavors of Three-State

 


EN\_L = 1  
 IN = x  
 OUT = Hi-Z

74x126

74x125
 
# Three-State Logic Circuit

- Normally, a logic circuit will not operate correctly if the outputs of two or more gates or other logic devices are directly connected to each other (multiple drivers conflict – “fighting”)
- Use of three-state logic permits the outputs of two or more gates or other logic devices to be connected together
- Data Selection Function:  
If  $S = 0$ ,  $OL = IN_0$ , else  $OL = IN_1$
- Performing data selection with 3-state buffers:




$$OL = IN_0 \cdot S' + IN_1 \cdot S$$

- Because  $EN_0 = S'$  and  $EN_1 = S$ , one of the two buffer outputs is always Hi-Z. (Recall: when a device output is Hi-Z, it “floats” as if it weren’t even there)

19 of 26
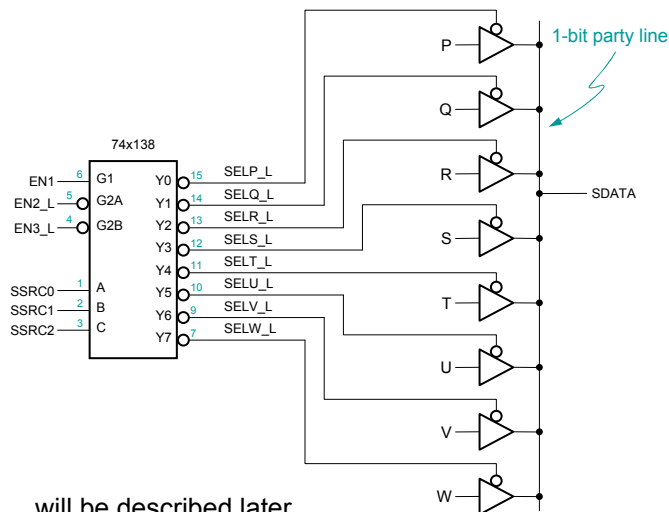
# 8 Sources Sharing a 3-state Party Line

We can tie multiple outputs together, if *at most one* at a time is driven.




a decoder circuit ... will be described later

20 of 26
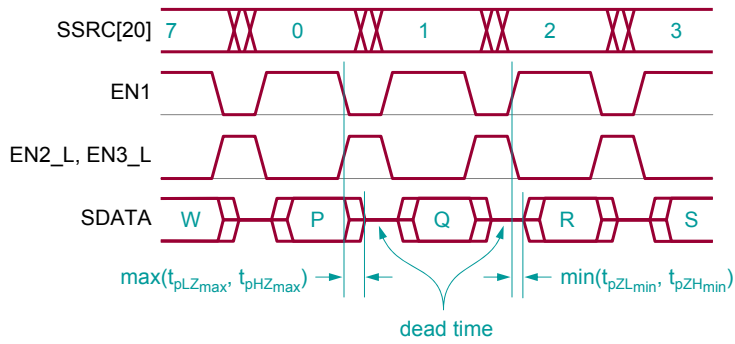
# Timing Considerations


Timing considerations for the three-state party line




21 of 26

# Three-State Drivers

octal three-state buffer  
logic symbol

 

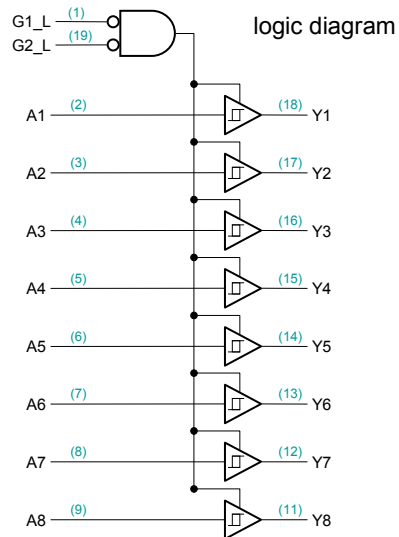
Note that enable inputs G1\_L and G2\_L simultaneously enable all eight buffers (i.e., all 8 inputs) — used in bus-based applications, described next ...



22 of 26

 
# Buses

- Tristate bus connecting multiple chips:



23 of 26


# Buses - Example

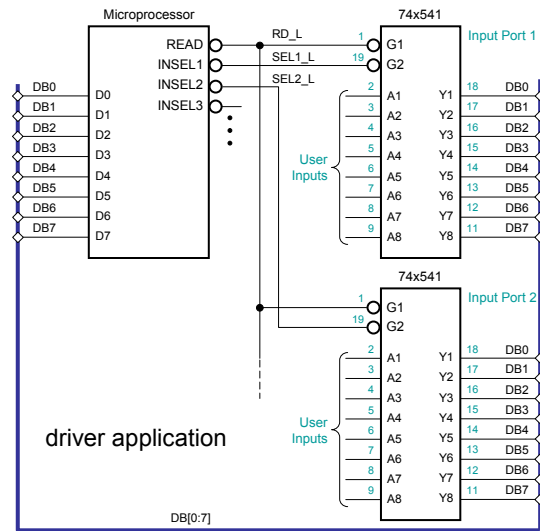

24 of 26


# Three-State Transceivers

logic diagram

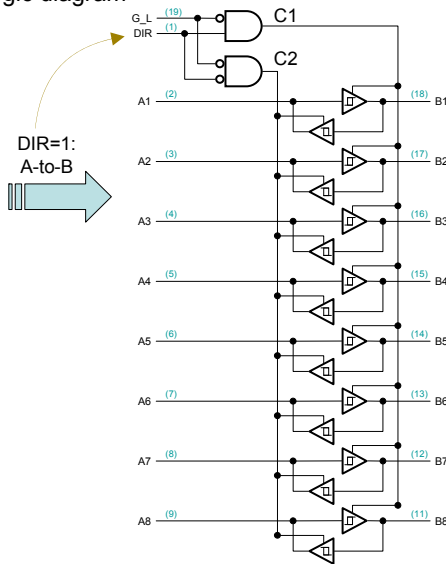

DIR=1:  
A-to-B

 octal three-state transceiver  
logic symbol




DIR=0:  
B-to-A

enable		direction	direction of transfer	
G_L	DIR		C1	C2
1	x	disconnected	0	0
0	0	B → A	0	1
0	1	A → B	1	0

25 of 26

# Transceiver Application

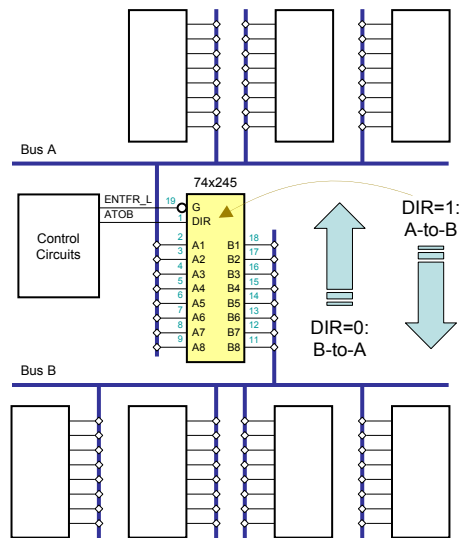Example use of bidirectional transceiver 74x245 to control the direction of data transfer on bidirectional buses



26 of 26